

ENEL434 Electronics II

No marks Homework

Given

$$S_{11} = 0.45 \angle 150^\circ,$$

$$S_{12} = 0.01 \angle -10^\circ,$$

$$S_{21} = 2.05 \angle 10^\circ,$$

$$S_{22} = 0.40 \angle 150^\circ$$

at $f = 10\text{GHz}$ and $Z_0 = 50\ \Omega$

- 1) Assume $Z_L = 50\ \Omega$ and find the length D_s of an open circuit stub and the length L_s of a transmission line that will conjugate match the input as shown in Figure 1. Always use the shortest length stub you can.
- 2) Now using the source matching network you found in (1), calculate the length D_o of the open circuit stub and length of the transmission line L_o that will conjugate match the output of the transistor as shown in Figure 2.

You may use Matlab to help calculate Γ_{in} and Γ_{out} and you will need to supply two Smith charts as part of your answer showing how you determined the length of stubs and lines. Smith charts are available on the courses folder (W:drive) under ENEL434.

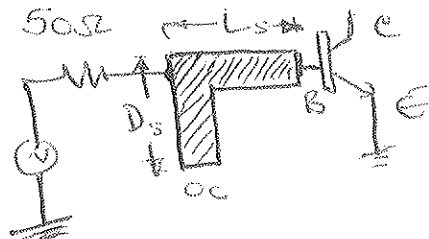


Fig 1 Input Matching Network.

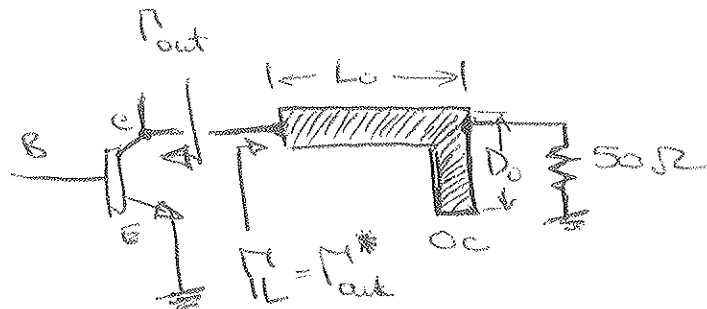


Fig 2 Output Matching Network.