

4. NOISE in RF CIRCUITS and SYSTEMS

ENEL434 Electronics 2

Summary

- Random variables (review)
- Noise basics
- Thermal noise
- Shot noise
- Flicker noise
- Circuit noise calculations
- Equivalent noise sources and noise temperature
- Representation of a noisy 2-port
- Noise figure and noise temperature
- Noise figure of an attenuator
- Cascaded communication system
- Examples

References

- D M Pozar, Microwave Engineering, 3rd Edition, John Wiley 2005 [Section 10.1]
- R E Collin, Foundations for Microwave Engineering, 2nd Edition, McGraw-Hill 1992 [Section 10.8]
- P Z Peebles, Jr, Probability, Random Variables and Random Signal Principles, 3rd Edition, McGraw-Hill 1993

Random Variables

Consider a **continuous random variable** X:

- It is **possible** for X to take any value on the range: $(-\infty, \infty)$
- The statistical behaviour is fully described by its **probability density function** $f(x)$.
- The **probability** that X is within the range $[a, b]$ is given by:

$$P(a \leq X \leq b) = \int_a^b f(x) dx$$

- Hence: $\int_{-\infty}^{\infty} f(x) dx = 1$
- The **mean** (or loosely average value) μ_x , and **variance** (spread) σ_x^2 are given by:

$$\mu_x = \int_{-\infty}^{\infty} x f(x) dx \quad \sigma_x^2 = \int_{-\infty}^{\infty} (x - \mu)^2 f(x) dx$$

Random Variables

Consider two **continuous random variables** X and Y:

- It is **possible** for X and Y to take any value on the range: $(-\infty, \infty)$
- The statistical behaviour of X and Y are fully described by their **joint probability density function** $f(x,y)$.
- The **probability** that X is within the range [a, b] AND Y is within the range [c, d] is given by:

$$P(a \leq X \leq b \cap c \leq Y \leq d) = \int_a^b \int_c^d f(x,y) dy dx$$

- Hence:

$$\int_{-\infty}^{\infty} \int_{-\infty}^{\infty} f(x,y) dy dx = 1$$

- X and Y are **independent** (outcome for X has no bearing on the outcome of Y) if $f(x,y) = f(x)f(y)$

Random Variables

Consider two **continuous random variables** X and Y:

- An important statistical property is the mean of the product XY called the **correlation**:

$$R_{XY} = \int_{-\infty}^{\infty} \int_{-\infty}^{\infty} xyf(x,y) dy dx$$

- If $R_{XY} = \mu_X \mu_Y$ then X and Y are **uncorrelated**.
- Independence of X and Y is sufficient to imply X and Y are uncorrelated. But the reverse statement is in general not true.

Random Variables

Consider the sum of multiple **independent continuous random variables**

$$Y = X_1 + X_2 + \dots + X_n$$

- The mean and variance of Y are:

$$\mu_Y = \mu_1 + \mu_2 + \dots + \mu_n$$

$$\sigma_Y^2 = \sigma_1^2 + \sigma_2^2 + \dots + \sigma_n^2$$

where μ_k and σ_k^2 are the mean and variance respectively of X_k

- Central Limit Theorem:** Y has a normal distribution as n tends to infinity regardless of the distributions of the components of Y ($X_1, X_2 \dots X_n$)
- If $X_1, X_2 \dots X_n$ all have normal distributions, then Y will have a normal distribution for any value of n

Noise Basics


- Noise is a random low level disturbance present in all real electrical circuits.

$$v(t) = v_{\text{Signal}}(t) + n(t)$$

- Noise becomes an issue when the level of the signal is comparable to $n(t)$.


- $n(t)$ is a **random process**. That is:

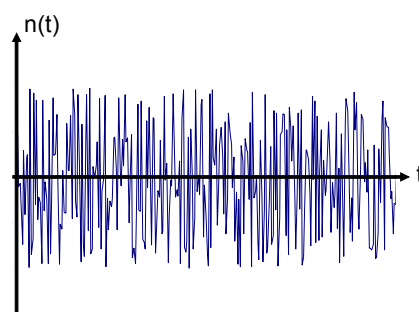- $n(t)$ is a random variable at time t
- $n(t_1)$ and $n(t_2)$ are a pair of random variables



Noise Basics

- $n(t)$ can be characterised by a probability density function at time t .
- That is we could consider an infinite number of realisations of the same noise process.
- The **mean μ_n of $n(t)$ is zero** for noise.
- The **variance σ_n^2 is non-zero** and is the noise power into a 1Ω resistor (since mean is zero).
- The correlation of $n(t_1)$ and $n(t_2)$, called **autocorrelation $R_{nn}(t_1, t_2)$** , is of interest.
- We assume that noise is the sum of many random events. Hence, $n(t)$ will have a **normal distribution**.
- Noise is called **white noise** if its power spectral density is constant.

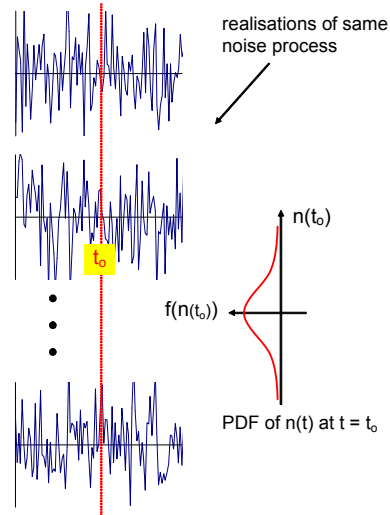

Noise Basics

- We may assume that the statistics are independent of time – ie **stationary**. In the case of autocorrelation dependent only on time difference.
- A useful assumption is that the noise source is **ergodic**.
- This means that the **statistics of $n(t)$ can be obtained from time averages of one realisation of $n(t)$** .

$$\mu_n = \langle n(t) \rangle = 0 \quad \langle n(t) \rangle = \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T n(t) dt$$

$$\sigma_n^2 = \langle (n(t) - \mu_n)^2 \rangle = \langle n(t)^2 \rangle \quad \langle n(t)^2 \rangle = \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T [n(t)]^2 dt$$

$$R_{nn}(t_1, t_2) = R_{nn}(\tau) = \langle n(t)n(t+\tau) \rangle$$

$$\langle n(t)n(t+\tau) \rangle = \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T n(t)n(t+\tau) dt$$

Noise Basics

- Another important aspect of $n(t)$ is its power spectral density $S_{nn}(\omega)$ and may be defined so that the power into a 1Ω resistor is given by:

$$P_{nn} = \frac{1}{2\pi} \int_{-\infty}^{\infty} S_{nn}(\omega) d\omega$$

- The power into 1Ω over a small bandwidth Δf centred at $f = \omega/2\pi$:

$$dP_{nn} = 2S_{nn}(\omega)\Delta f$$

- It can be shown that

$$S_{nn}(\omega) = \int_{-\infty}^{\infty} R_{nn}(\tau) e^{-j\omega\tau} d\tau$$

- It can be shown that:

- R_{nn} is maximum at $\tau = 0$
- R_{nn} is even, so therefore, **S_{nn} is pure real and an even function.**

Noise Basics

Say that we have two noise sources $n_1(t)$ and $n_2(t)$.

- The **cross-correlation** is given by:

$$R_{n_1n_2}(\tau) = \langle n_1(t)n_2(t+\tau) \rangle$$

- The **cross-power spectral density** is:

$$S_{n_1n_2}(\omega) = \int_{-\infty}^{\infty} R_{n_1n_2}(\tau) e^{-j\omega\tau} d\tau$$

- Unlike autocorrelation, cross-correlation is in general not even, and hence the cross-power spectral density is in general complex.
- $\text{Re}S_{n_1n_2}$ is an even function, $\text{Im}S_{n_1n_2}$ is an odd function.
- The cross-power into 1Ω over a small bandwidth Δf centred at $f = \omega/2\pi$:

$$dP_{n_1n_2} = 2\text{Re}(S_{n_1n_2}(\omega))\Delta f$$

Thermal Noise

- In a conducting material, thermal energy manifests itself as random vibration of atoms and random motion of electrons.
- The electrons have thermal velocities significantly higher than drift velocity.
- The random motion of the electrons gives rise to a noise voltage across and noise current through the conductor.
- This noise is called thermal noise, or Johnson noise or Nyquist noise.
- **Mean-square** Thevenin voltage of a resistor with resistance R is:

$$\langle v_n(t)^2 \rangle = \frac{4hfBR}{e^{hf/kT} - 1}$$

where $h = 6.626 \times 10^{-34}$ Js (Planck's constant)


$k = 1.38 \times 10^{-23}$ J/K (Boltzmann's constant)

T is absolute temperature (K)

f is the centre frequency (Hz) of the system whose bandwidth is B (Hz)

Thermal Noise

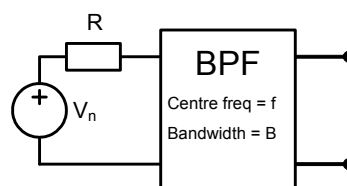
$$\langle v_n(t)^2 \rangle = \frac{4hfBR}{e^{hf/kT} - 1}$$



- Up to about 1000 GHz thermal noise is white: $\langle v_n(t)^2 \rangle \approx 4kTBR$
- The power spectral density of V_n is: $S_{V_n V_n}(\omega) = 2kTR$
- The noise power into bandwidth Δf is: $dP_{v_n v_n} = d\langle v_n(t)^2 \rangle = 4kTR \Delta f$
- A Norton equivalent is also possible.

Thermal Noise
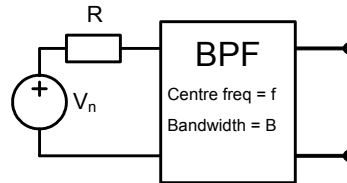
$$\langle v_n(t)^2 \rangle = \frac{4hfBR}{e^{hf/kT} - 1}$$




Because the resistor can be represented by a generator:

- Available power: $P = kTB$
- Available power spectral density: $S(\omega) = \frac{kT}{2}$

Thermal Noise
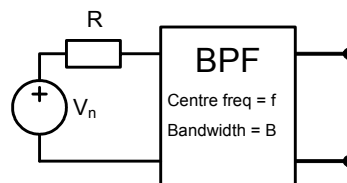
$$\langle v_n(t)^2 \rangle = \frac{4hfBR}{e^{hf/kT} - 1} \approx 4kTBR$$



- eg. $T = 300 \text{ K}$, $B = 100 \text{ MHz}$, $N = 0.414 \text{ pW} \equiv -93.8 \text{ dBm}$
- Often engineers immerse circuitry in liquid nitrogen or even liquid helium to lower T and hence noise voltage.

Shot Noise

- Shot noise is present in semiconductor devices when conducting current.
- The current of a pn junction for example, involves the passage minority carriers across the pn junction – which are random events.
- For a junction with DC current I_o , the mean-square noise current into bandwidth B is given by:

$$\langle i_n^2 \rangle = 2qI_oB$$

where $q = 1.6 \times 10^{-19} \text{ C}$

and the power spectral density is given by: $S_{i_{nn}}(\omega) = qI_o$

- Shot noise is white.
- eg. for $I_o = 10 \text{ mA}$ and $B = 100 \text{ MHz}$, $\langle i_n^2 \rangle = 0.32 \times 10^{-12} \text{ A}^2$

Flicker or 1/f Noise

- Flicker noise is present in all semiconductor devices and resistive elements.
- Like Shot noise, Flicker noise is associated with current flow.
- Various origins but is essentially the result of contamination and defects present in manufacturing processes.
- Flicker noise is NOT white and nor is it Gaussian.
- The power spectral density of the noise current is given by:

$$S_{i_{nn}}(\omega) = K \frac{I_o^a}{\omega^b}$$

where K, a and b are process / technology dependent constants.

a is typically in the range 0.5 to 2

b is around unity – hence “1/f” noise

- Flicker noise is negligible in microwave amplifiers but Flicker noise can be up-converted in nonlinear microwave circuits such as mixers and oscillators.

Equivalent Noise Sources

- More often in microwave and RF engineering we are interested in the level of noise and not its physical origin.
- In this case, we would represent the noise source by an equivalent thermal noise source.
- **eg.** Suppose that the available noise power from an antenna is 0.1pW into a bandwidth of 100 MHz.

The available noise power N from a resistor at temperature T_e is:

$$N = kT_e B$$

Hence to achieve $N = 0.1$ pW into $B = 100$ MHz, T_e needs to be 72 K.

ie. taking a resistor and cooling it to -201°C would achieve the same noise power.

Circuit Noise Calculations


eg. Calculate the equivalent noise voltage of two noise voltages in series.

From a **time-domain** point of view ...

$$\begin{aligned}\langle v_{nT}(t)^2 \rangle &= \langle (v_{n1}(t) + v_{n2}(t))^2 \rangle \\ &= \langle v_{n1}^2 + v_{n2}^2 + 2v_{n1}v_{n2} \rangle \\ &= \langle v_{n1}^2 \rangle + \langle v_{n2}^2 \rangle + 2\langle v_{n1}v_{n2} \rangle\end{aligned}$$

$$\text{where } \langle v_{n1}v_{n2} \rangle = \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T v_{n1}(t)v_{n2}(t)dt$$
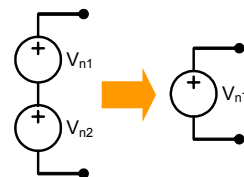
$$\langle v_{n1}v_{n2} \rangle = 0 \text{ for independent noise sources. Why?}$$



Circuit Noise Calculations

eg. Calculate the equivalent noise voltage of two noise voltages in series.


From a **spectral domain** point of view ...

$$V_{nT} = V_{n1} + V_{n2}$$

$$|V_{nT}|^2 = |V_{n1} + V_{n2}|^2 = |V_{n1}|^2 + |V_{n2}|^2 + 2\text{Re}[V_{n1}V_{n2}^*]$$

For **deterministic signals into 1 Ω** :

- $|V_{nT}|^2$ is the power of source V_{nT}
- $|V_{n1}|^2$ is the power of source V_{n1}
- $|V_{n2}|^2$ is the power of source V_{n2}
- $\text{Re}(V_{n1}V_{n2}^*)$ is a "cross-power"

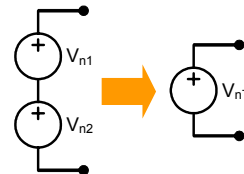

Circuit Noise Calculations

eg. Calculate the equivalent noise voltage of two noise voltages in series.

From a **spectral domain** point of view ...

$$V_{nT} = V_{n1} + V_{n2}$$

$$|V_{nT}|^2 = |V_{n1} + V_{n2}|^2 = |V_{n1}|^2 + |V_{n2}|^2 + 2\text{Re}[V_{n1}V_{n2}^*]$$

For **noise signals into 1 Ω over bandwidth Δf** :


$2S_{V_{nT}V_{nT}}\Delta f$ is the power from source V_{nT}

$2S_{V_{n1}V_{n1}}\Delta f$ is the power from source V_{n1}

$2S_{V_{n2}V_{n2}}\Delta f$ is the power from source V_{n2}

$2\text{Re}(S_{V_{n1}V_{n2}})\Delta f$ is the cross-power from sources V_{n1} and V_{n2} noting that
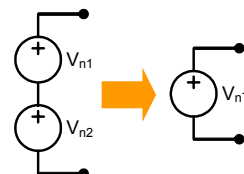
$$\text{Re}(S_{V_{n1}V_{n2}}(-\omega)) = \text{Re}(S_{V_{n1}V_{n2}}(\omega))$$



Circuit Noise Calculations


eg. Calculate the equivalent noise voltage of two noise voltages in series.

From a **spectral domain** point of view ...

$$|V_{nT}|^2 = |V_{n1} + V_{n2}|^2 = |V_{n1}|^2 + |V_{n2}|^2 + 2\text{Re}[V_{n1}V_{n2}^*]$$


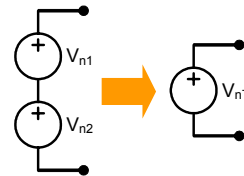
$$2S_{V_{nT}V_{nT}}\Delta f = 2S_{V_{n1}V_{n1}}\Delta f + 2S_{V_{n2}V_{n2}}\Delta f + 4\text{Re}(S_{V_{n1}V_{n2}})\Delta f$$



Circuit Noise Calculations

eg. Calculate the equivalent noise voltage of two noise voltages in series.

From a **spectral domain** point of view ...


V_{n1} and V_{n2} can be described by their:

- auto-correlations \leftrightarrow power spectral densities
- cross-correlation \leftrightarrow cross power spectral density

$$2S_{V_{nT}V_{nT}}\Delta f = 2S_{V_{n1}V_{n1}}\Delta f + 2S_{V_{n2}V_{n2}}\Delta f + 4\text{Re}(S_{V_{n1}V_{n2}})\Delta f$$


$$R_{V_{n1}V_{n2}} = \langle v_{n1}(t)v_{n2}(t+\tau) \rangle$$
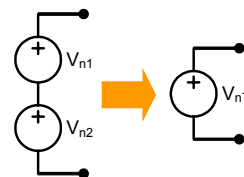
$$S_{V_{n1}V_{n2}}(\omega) = \int_{-\infty}^{\infty} R_{V_{n1}V_{n2}}(\tau)e^{-j\omega\tau}d\tau$$




Representation of a Noisy 2-Port

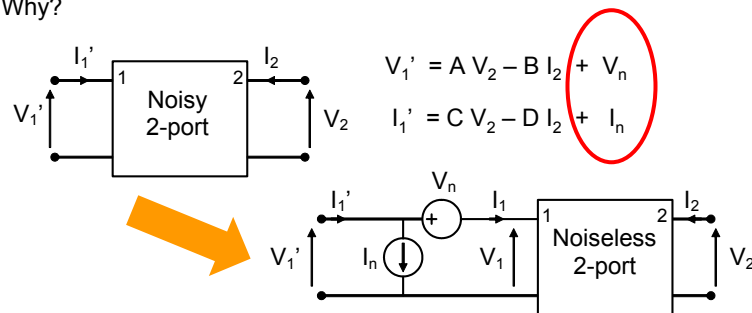- The 2-port could be a transistor, an amplifier, a coaxial cable etc.
- Due to the physical processes inherent in the 2-port, the 2-port will be noisy.
- We know that from circuit analysis that the terminal behaviour of a 2-port can be described by ABCD parameters in the frequency (spectral) domain.
- We include two noise sources at the input. These sources are correlated. Why?




Representation of a Noisy 2-Port

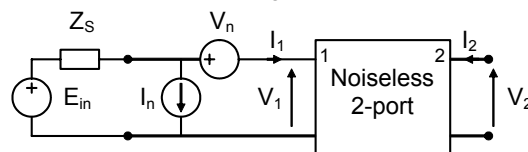- We would normally connect a generator (Thevenin voltage E_{in} and impedance Z_S) to the input of the noisy-two port.
- The generator supplies the input signal and input noise (effectively due to $\text{Re}Z_S$).



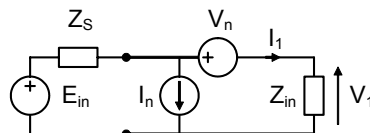- Let us consider the input part of the circuit:




where Z_{in} is the input impedance to the 2-port and will be a function of load connected to port 2.

Representation of a Noisy 2-Port

Let us analyse the input part of the circuit.

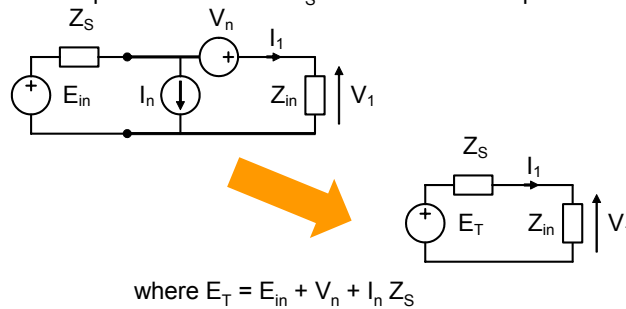- We can arbitrarily change the polarity of V_n .
- We can lump the sources and Z_S into its Thevenin equivalent:



Representation of a Noisy 2-Port

- The power available from the equivalent generator is:

$$E_T = E_{in} + V_n + I_n Z_S$$

$$P_A = \frac{|E_T|^2}{4 \operatorname{Re} Z_S}$$

- The square of $|E_T|$ is:

$$|E_T|^2 = |E_{in} + V_n + I_n Z_S|^2 = |E_{in}|^2 + |V_n|^2 + |I_n|^2 |Z_S|^2 + 2 \operatorname{Re}[E_{in}(V_n + I_n Z_S)^*] + 2 \operatorname{Re}[V_n(I_n Z_S)^*]$$

$$2S_{E_T E_T} \Delta f = 2S_{E_{in} E_{in}} \Delta f + 2S_{V_n V_n} \Delta f + 2|Z_S|^2 S_{I_n I_n} \Delta f + 4 \operatorname{Re}(S_{E_{in} V_n}) \Delta f + 4 \operatorname{Re}(S_{E_{in} I_n} Z_S^*) \Delta f + 4 \operatorname{Re}(S_{V_n I_n} Z_S^*) \Delta f$$

Representation of a Noisy 2-Port

- Note that above we use the result that:

$$\operatorname{Re}(S_{v_n l_n}(-\omega)Z_S^*(-\omega)) = \operatorname{Re}(S_{v_n l_n}^*(\omega)Z_S(\omega)) = \operatorname{Re}(S_{v_n l_n}(\omega)Z_S^*(\omega))$$

as well as the other properties of power spectral density functions.

- E_{in} is uncorrelated with V_n and I_n

$$2S_{E_T E_T} \Delta f = 2S_{E_{in} E_{in}} \Delta f + 2S_{V_n V_n} \Delta f + 2|Z_S|^2 S_{I_n I_n} \Delta f \\ + 4\operatorname{Re}(S_{E_{in} V_n}) \Delta f + 4\operatorname{Re}(S_{E_{in} I_n} Z_S^*) \Delta f + 4\operatorname{Re}(S_{V_n I_n} Z_S^*) \Delta f$$



$$2S_{E_T E_T} \Delta f = 2S_{E_{in} E_{in}} \Delta f + 2S_{V_n V_n} \Delta f + 2|Z_S|^2 S_{I_n I_n} \Delta f \\ + 4\operatorname{Re}(S_{V_n I_n}) \operatorname{Re}(Z_S) \Delta f + 4\operatorname{Im}(S_{V_n I_n}) \operatorname{Im}(Z_S) \Delta f$$

Representation of a Noisy 2-Port

- Finally:

$$2S_{E_T E_T} \Delta f = 2S_{E_{in} E_{in}} \Delta f + 2S_{V_n V_n} \Delta f + 2|Z_S|^2 S_{I_n I_n} \Delta f \\ + 4\operatorname{Re}(S_{V_n I_n}) \operatorname{Re}(Z_S) \Delta f + 4\operatorname{Im}(S_{V_n I_n}) \operatorname{Im}(Z_S) \Delta f$$



$$2S_{E_T E_T} \Delta f = 2\Delta f \left[S_{E_{in} E_{in}} + a + b|Z_S|^2 + c \operatorname{Re} Z_S + d \operatorname{Im} Z_S \right]$$

where a, b, c and c are real constants related to the noise properties of the 2-port network

Noise Figure and Noise Temperature

- Noise figure (F) is a figure of merit of a 2-port element (such as an amplifier or down-converter).
- The signal to noise ratio always deteriorates through its passage of linear processes.

- **F measures this deterioration of SNR:**

$$F = \frac{\text{SNR}_{\text{input}}}{\text{SNR}_{\text{output}}}$$

- **A low F is better than a high F. The best F we could ever obtain is 1.**
- We normally talk about available powers:
 - S_{input} is the signal power available from the input generator
 - S_{output} is the signal power available at the output of the 2-port
 - N_{input} is the noise power available from the generator
 - N_{output} is the noise power available at the output of the 2-port

Noise Figure and Noise Temperature

- The 2-port will amplify (or attenuate) the input signal and noise.
- The 2-port will contribute noise.
- We can refer this contributed noise to the input of the 2-port so that it is amplified (or attenuated) by the 2-port.

- $S_{\text{output}} = G_A S_{\text{input}}$

where G_A is the available power gain of the 2-port

- $N_{\text{output}} = G_A N_{\text{input}} + G_A N_{\text{added}}$

where N_{added} is the noise added by the 2-port REFERED to its input

- Hence:

$$F = \frac{N_{\text{input}} + N_{\text{added}}}{N_{\text{input}}} = 1 + \frac{N_{\text{added}}}{N_{\text{input}}}$$

- nb. F is a power ratio so $F_{\text{dB}} = 10 \log_{10} F$

Noise Figure and Noise Temperature

- Earlier we talked about equivalent noise source as though the origin of all noise is thermal.
- ie $N = kTB$ where T is the effective noise temperature.
- $N_{\text{input}} = kT_S B$ where T_S is the effective noise temperature of the generator.
- $N_{\text{added}} = kT_e B$ where T_e is the effective noise temperature of the 2-port referred to its input port.
- Hence:

$$F = 1 + \frac{N_{\text{added}}}{N_{\text{input}}} = 1 + \frac{T_e}{T_S}$$

Noise Figure and Noise Temperature

$$F = 1 + \frac{N_{\text{added}}}{N_{\text{input}}} = 1 + \frac{T_e}{T_S}$$

- T_e is a parameter of the 2-port. T_S is a parameter of the generator.
- Suppose we have an amplifier whose T_e is 290 K.
 - Salesman A sets $T_S = 290$ K and hence advertises amplifier $F = 2$
 - Salesman B sets $T_S = 2900$ K and hence advertises amplifier $F = 1.1$
 - Clearly Salesman B gets the most sales
 - Do you see the dilemma the customer faces when F is specified?
- **For this reason whenever you calculate, write or read F it is understood that $T_S = 290$ K ($\equiv 17^\circ\text{C}$).**

$$F = 1 + \frac{T_e}{290}$$

Noise Figure and Noise Temperature

- Recall:

$$\underbrace{\frac{2S_{E_T E_T} \Delta f}{4 \operatorname{Re} Z_S}}_{N_{\text{total}}} = \underbrace{\frac{2S_{E_{in} E_{in}} \Delta f}{4 \operatorname{Re} Z_S}}_{N_{\text{input}}} + \underbrace{\frac{2\Delta f}{4 \operatorname{Re} Z_S} (a + b|Z_S|^2 + c \operatorname{Re} Z_S + d \operatorname{Im} Z_S)}_{N_{\text{added}}}$$

- Assuming that $2S_{E_{in} E_{in}} \Delta f$ is effectively thermal due to $\operatorname{Re} Z_S$ with effective temperature $T_S (= 290)$:

$$\underbrace{\frac{2S_{E_T E_T} \Delta f}{4 \operatorname{Re} Z_S}}_{N_{\text{total}}} = \underbrace{\frac{2\Delta f (2k \times 290 \times \operatorname{Re} Z_S)}{4 \operatorname{Re} Z_S}}_{N_{\text{input}}} + \underbrace{\frac{2\Delta f}{4 \operatorname{Re} Z_S} (a + b|Z_S|^2 + c \operatorname{Re} Z_S + d \operatorname{Im} Z_S)}_{N_{\text{added}}}$$

Noise Figure and Noise Temperature

- Hence:

$$F = \frac{N_{\text{input}} + N_{\text{added}}}{N_{\text{input}}} = 1 + \frac{\alpha |Z_S|^2 + \beta \operatorname{Re} Z_S + \gamma \operatorname{Im} Z_S + \epsilon}{\operatorname{Re} Z_S}$$

where α , β , γ and ϵ are real constants related to the noise properties of the 2-port network

- With some algebraic manipulation:

$$F = F_{\min} + G_m \frac{|Z_S - Z_{\text{opt}}|^2}{\operatorname{Re} Z_S}$$

where F_{\min} is the minimum noise figure

Z_{opt} is the generator impedance that minimises F , and

G_m is a proportionality constant with dimensions conductance.

- nb. G_m is not a physical conductance

Noise Figure and Noise Temperature

But:

$$\Gamma_S = \frac{Z_S - Z_o}{Z_S + Z_o} \quad \Gamma_{opt} = \frac{Z_{opt} - Z_o}{Z_{opt} + Z_o}$$

where Z_o is the reference impedance for reflection coefficient and S-parameters. Substitution into:

$$F = F_{min} + G_m \frac{|Z_S - Z_{opt}|^2}{\text{Re} Z_S}$$

yields:

$$F = F_{min} + \frac{4R_n}{Z_o} \frac{|\Gamma_S - \Gamma_{opt}|^2}{(1 - |\Gamma_S|^2)|1 + \Gamma_{opt}|^2}$$

where F_{min} is the minimum noise figure

Γ_{opt} is the value of Γ_S that minimises F , and

R_n is a proportionality constant called the “noise resistance” and is NOT a physical resistance.

Noise Figure and Noise Temperature

$$F = F_{min} + \frac{4R_n}{Z_o} \frac{|\Gamma_S - \Gamma_{opt}|^2}{(1 - |\Gamma_S|^2)|1 + \Gamma_{opt}|^2}$$

- The above expressions tell us how F varies with choice of Γ_S
- Recall that gain is also dependent on Γ_S
- This means that amplifier design requires trade-off of gain and F
- Fortunately ultra-low noise transistors are designed so that:
 - Γ_S in the vicinity of Γ_{opt} is associated with high gain
 - R_n is low so that F increases at a low rate as Γ_S moves away from Γ_{opt}

Example

Fujitsu *High Electron Mobility Transistor* (HEMT): FHX14X

Source: www.eudyna.com

At $V_{DS} = 2 \text{ V}$, $I_D = 10 \text{ mA}$, 20 GHz and ambient temperature of 25°C :

$$S_{11} = 0.523 / -140.0^\circ \quad S_{12} = 0.133 / 58.4^\circ$$

$$S_{21} = 2.314 / 70.8^\circ \quad S_{22} = 0.335 / -59.4^\circ$$

$$\Gamma_{\text{opt}} = 0.52 / 136^\circ \quad \frac{R_N}{Z_o} = 0.07 \quad F_{\text{min}} = 1.03 \text{ dB} = 1.268$$


What is the noise figure if simultaneous conjugate matching is used?

With $\Gamma_S = 0.835 / 146^\circ$ the noise figure is:

$$F = F_{\text{min}} + \frac{4R_N}{Z_o} \frac{|\Gamma_S - \Gamma_{\text{opt}}|^2}{(1 - |\Gamma_S|^2)(1 + |\Gamma_{\text{opt}}|^2)} = 1.268 + 4 \times 0.07 \times \frac{|0.835 / 146^\circ - 0.52 / 136^\circ|^2}{(1 - 0.835^2)(1 + 0.52^2)} = 1.466 \approx 1.66 \text{ dB}$$

Noise Figure of an Attenuator

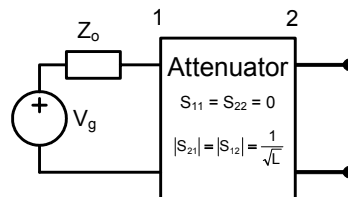
Consider an attenuator with matched ports and driven by a matched generator (reference impedance Z_o is also pure real):



- We assume that the generator and attenuator are at temperature T .
- Hence, $N_{\text{in}} = kTB$
- Looking into port 2 – the equivalent is a generator with Thevenin impedance Z_o and we would expect it to have a noise temperature of T .
- Hence, $N_o = kTB$

Noise Figure of an Attenuator

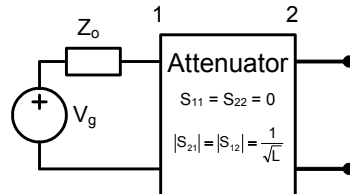
Consider an attenuator with matched ports and driven by a matched generator (reference impedance Z_o is also pure real):



- But: $N_o = \frac{1}{L}(N_{in} + N_{added}) = \frac{1}{L}(kTB + N_{added})$
- Hence: $N_{added} = (L - 1) kTB = kT_e B$
where $T_e = (L - 1)T$

Noise Figure of an Attenuator

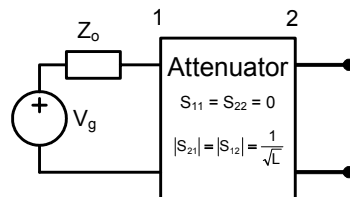Consider an attenuator with matched ports and driven by a matched generator (reference impedance Z_o is also pure real):




- Using the relationship for F ($= 1 + T_e/290$):

$$F = 1 + (L - 1) \frac{T}{290}$$

- This means that **F is equal to its insertion loss L when it has a physical temperature of 290 K.**

Cascaded Communication System

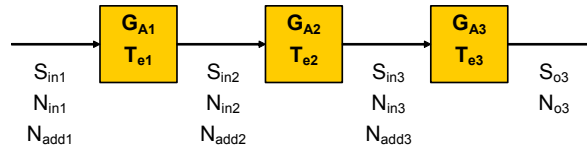Consider a 3-stage communications system with signal (S) and noise (N) powers as indicated:




We make the assumption that over the bandwidth B:

- Thermal noise models can be used. eg:
 - $N_{in1} = kT_S B$ where T_S is the noise temperature of the input source
 - $N_{add1} = kT_{e1} B$
- T_S, T_{e1}, G_{A1} etc are flat

Cascaded Communication System

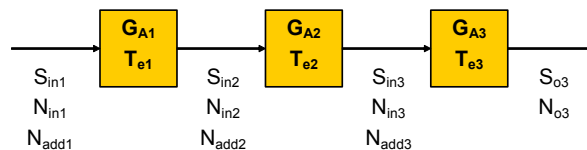Consider a 3-stage communications system with signal (S) and noise (N) powers as indicated:



Considering the signal powers:

$$S_{in2} = G_{A1} S_{in1}$$


$$S_{in3} = G_{A2} S_{in2} = G_{A1} G_{A2} S_{in1}$$

$$S_{o3} = G_{A3} S_{in3} = G_{A1} G_{A2} G_{A3} S_{in1}$$

So the **overall available gain is $G_A = G_{A1} G_{A2} G_{A3}$**

Cascaded Communication System

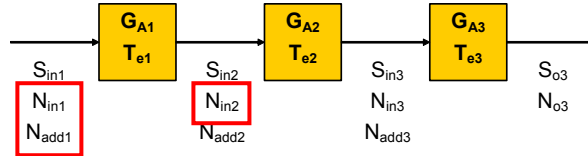Consider a 3-stage communications system with signal (S) and noise (N) powers as indicated:



Considering the noise powers:

$$N_{in1} = kT_S B \quad \text{where } T_S \text{ is the noise temperature of the input source}$$


$$N_{add1} = kT_{e1} B$$

$$N_{in2} = G_{A1}(N_{in1} + N_{add1})$$

$$= kG_{A1}(T_S + T_{e1})B$$

Cascaded Communication System

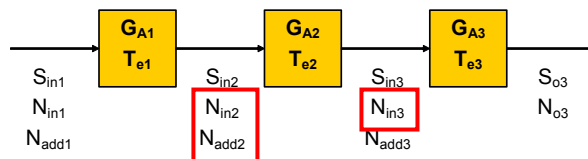Consider a 3-stage communications system with signal (S) and noise (N) powers as indicated:



Considering the noise powers:

$$N_{in2} = kG_{A1}(T_S + T_{e1})B$$


$$N_{add2} = kT_{e2} B$$

$$N_{in3} = G_{A2}(N_{in2} + N_{add2})$$

$$= kG_{A1}G_{A2}(T_S + T_{e1})B + kG_{A2}T_{e2}B$$

Cascaded Communication System

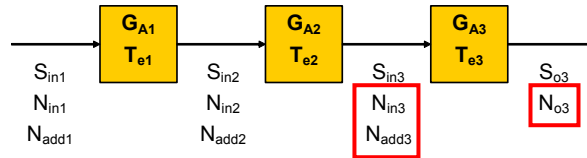Consider a 3-stage communications system with signal (S) and noise (N) powers as indicated:



Considering the noise powers:

$$N_{in3} = kG_{A1}G_{A2}(T_S + T_{e1})B + kG_{A2}T_{e2}B$$


$$N_{add3} = kT_{e3}B$$

$$N_{o3} = G_{A3}(N_{in3} + N_{add3})$$

$$= k[G_{A1}G_{A2}G_{A3}(T_S + T_{e1}) + G_{A2}G_{A3}T_{e2} + G_{A3}T_{e3}]B$$

Cascaded Communication System

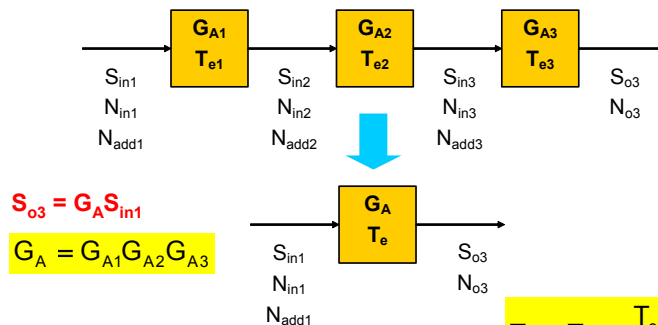Consider a 3-stage communications system with signal (S) and noise (N) powers as indicated:




$$N_{o3} = kG_A(T_S + T_e)B$$

$$= k[G_{A1}G_{A2}G_{A3}(T_S + T_{e1}) + G_{A2}G_{A3}T_{e2} + G_{A3}T_{e3}]B$$

Cascaded Communication System

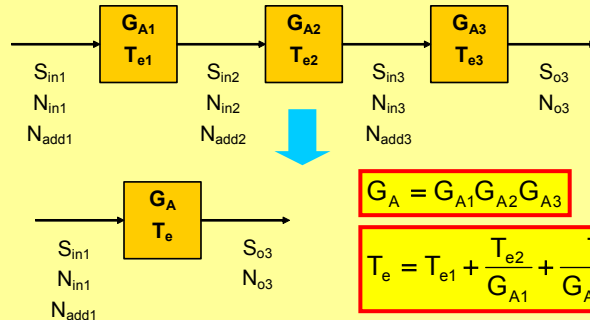
Consider a 3-stage communications system with signal (S) and noise (N) powers as indicated:



- The result for T_e is significant as it says that the **first stage has the most impact on system noise performance**.
- Modification of formulae for different number of stages should be apparent

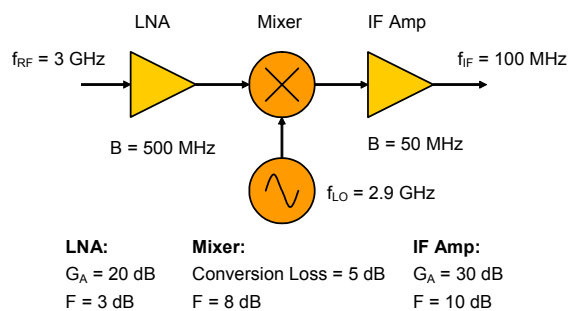Example 1


Calculate the gain and noise figure of the following system:



- **The block with the narrowest bandwidth determines B for noise calculations.** Hence $B = 50 \text{ MHz}$.
- Although the mixer employs a nonlinear element, the down-conversion process is linear provided input signal is small-signal.

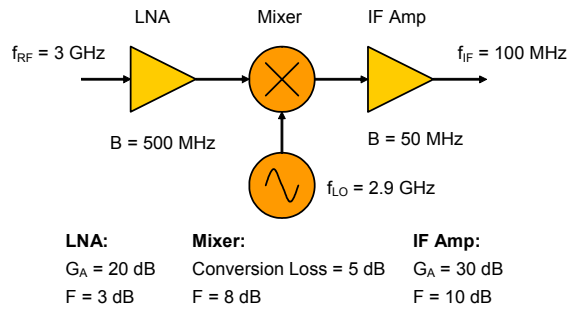Example 1

Calculate the gain and noise figure of the following system:



$$G_{A1} = 20 \text{ dB} = \mathbf{100}$$

$$F_1 = 3 \text{ dB} = \mathbf{2}$$

$$G_{A2} = -5 \text{ dB} = \mathbf{0.316}$$

$$F_2 = 8 \text{ dB} = \mathbf{6.31}$$

$$G_{A3} = 30 \text{ dB} = \mathbf{1000}$$

$$F_3 = 10 \text{ dB} = \mathbf{10}$$

Example 1

$$G_{A1} = 20 \text{ dB} = \mathbf{100}$$

$$F_1 = 3 \text{ dB} = \mathbf{2}$$

$$G_{A2} = -5 \text{ dB} = \mathbf{0.316}$$

$$F_2 = 8 \text{ dB} = \mathbf{6.31}$$

$$G_{A3} = 30 \text{ dB} = \mathbf{1000}$$

$$F_3 = 10 \text{ dB} = \mathbf{10}$$

$$T_{e1} = 290(2 - 1) \\ = 290 \text{ K}$$

$$T_{e2} = 290(6.31 - 1) \\ = 1540 \text{ K}$$

$$T_{e3} = 290(10 - 1) \\ = 2610 \text{ K}$$

$$G_A = G_{A1} G_{A2} G_{A3} \\ = 100 \times 0.316 \times 1000 \\ = 31600 \\ \equiv \mathbf{45 \text{ dB}}$$

Example 1

$$G_{A1} = 20 \text{ dB} = 100$$

$$G_{A2} = -5 \text{ dB} = 0.316$$

$$G_{A3} = 30 \text{ dB} = 1000$$

$$F_1 = 3 \text{ dB} = 2$$

$$F_2 = 8 \text{ dB} = 6.31$$

$$F_3 = 10 \text{ dB} = 10$$

$$T_{e1} = 290(2 - 1) \\ = 290 \text{ K}$$

$$T_{e2} = 290(6.31 - 1) \\ = 1540 \text{ K}$$


$$T_{e3} = 290(10 - 1) \\ = 2610 \text{ K}$$

$$T_e = T_{e1} + \frac{T_{e2}}{G_{A1}} + \frac{T_{e3}}{G_{A1}G_{A2}} \\ = 290 + \frac{1540}{100} + \frac{2610}{100 \times 0.316} \\ = 290 + 15.4 + 83 \text{ K} \\ = 388 \text{ K}$$

$$F = 1 + \frac{T_e}{290} \\ = 1 + \frac{388}{290} \\ = 2.34 \\ \equiv 3.7 \text{ dB}$$

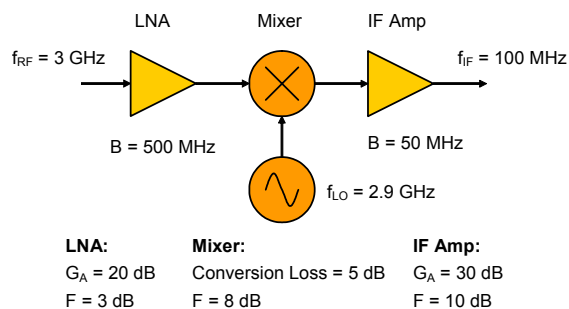Example 2

Calculate the minimum input signal power so that the output SNR is greater than 15 dB when the input source has a noise temperature of 100 K.



We know from the previous example:

$$T_e = 388 \text{ K} \quad G_A = 31600 \quad \text{and} \quad B = 50 \text{ MHz}$$

Example 2

Output signal power:

$$S_o = G_A S_{in}$$

Output noise power:

$$N_o = k(T_e + T_s)BG_A$$

Output SNR:

$$SNR_o = \frac{G_A S_{in}}{k(T_e + T_s)BG_A}$$

Hence:

$$\begin{aligned} S_{in} &= k(T_e + T_s)B SNR_o \\ &= 1.38 \times 10^{-23} (388 + 100) 50 \times 10^6 \times 31.6 \\ &= 1.064 \times 10^{-11} \text{ W} \\ &\equiv -80 \text{ dBm} \end{aligned}$$

Example 2

Note the input SNR:

$$\begin{aligned} SNR_{in} &= \frac{S_{in}}{kT_s B} \\ &= \frac{1.064 \times 10^{-11}}{1.38 \times 10^{-23} \times 100 \times 50 \times 10^6} \\ &= 154 \\ &\equiv 22 \text{ dB} \end{aligned}$$

Example 3

You are to design a satellite TV receiver front-end low-noise block (LNB) and integrate it with the antenna which is to be located outdoors and 5 m away from the indoor unit (containing mixer, IF amp, decoder etc).

Specifications and considerations include:

- Centre frequency = 11.4 GHz
- Bandwidth = 300 MHz
- Maximum noise figure of 4 dB
- Minimum gain of 55 dB
- Antenna is to be located 5 m away from the indoor unit
- Indoor unit contains down-converter, IF amplifier, decoder etc.
- The box to contain outdoor electronics needs to be weather proof and its cost increases with size.

Example 3


You are restricted to use the following:

- 1 x Antenna: $T_e = 150 \text{ K}$
- 2 x Amplifier: $G_A = 40 \text{ dB}$ $F = 2 \text{ dB}$
- 1 x Coaxial cable: Length = 5 m Loss = 20 dB

- The low noise block can therefore use two amplifiers and there will be a coaxial cable connecting the antenna / outdoor unit to the indoor unit.
- The issues are whether we have electronics (amplifier(s)) outside in an outdoor unit or place them in the indoor unit.
- The overall gain of the two amplifiers and the coaxial cable is 60 dB thereby satisfying the gain specification.
- The overall gain does not depend on what order the these blocks are arranged.


Example 3

There are three possible combinations:

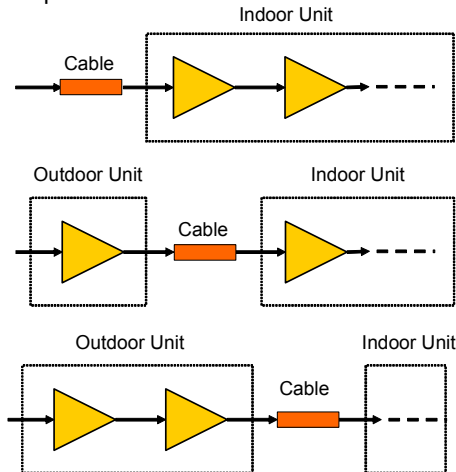

Example 3

Let us consider the first possibility:

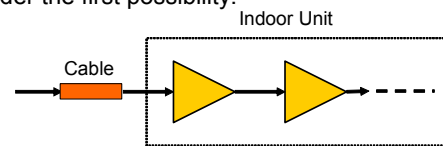

$$G_{A1} = -20 \text{ dB} \equiv 0.01$$

$$F_1 = 20 \text{ dB} \equiv 100$$

$$T_{e1} = 28710 \text{ K}$$

$$G_{A2} = 40 \text{ dB} \equiv 10^4$$

$$F_2 = 2 \text{ dB} \equiv 1.58$$

$$T_{e2} = 170 \text{ K}$$

$$G_{A3} = 40 \text{ dB} \equiv 10^4$$

$$F_3 = 2 \text{ dB} \equiv 1.58$$


$$T_{e3} = 170 \text{ K}$$

$$T_e = T_{e1} + \frac{T_{e2}}{G_{A1}} + \frac{T_{e3}}{G_{A1}G_{A2}} = 28710 + \frac{170}{0.01} + \frac{170}{0.01 \times 10^4} = 45710 \text{ K}$$

$$F = 1 + \frac{T_e}{290} = 1 + \frac{45710}{290} = 159 \equiv 22 \text{ dB} \quad \text{Cheap but bad!!}$$

Example 3

Let us consider the second possibility:

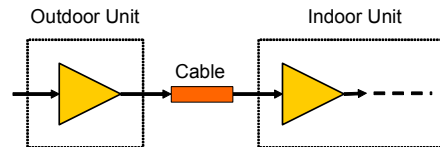

$$G_{A1} = 40 \text{ dB} \equiv 10^4$$

$$F_1 = 2 \text{ dB} \equiv 1.58$$

$$T_{e1} = 170 \text{ K}$$

$$G_{A2} = -20 \text{ dB} \equiv 0.01$$

$$F_2 = 20 \text{ dB} \equiv 100$$

$$T_{e2} = 28710 \text{ K}$$

$$G_{A3} = 40 \text{ dB} \equiv 10^4$$

$$F_3 = 2 \text{ dB} \equiv 1.58$$

$$T_{e3} = 170 \text{ K}$$

$$T_e = T_{e1} + \frac{T_{e2}}{G_{A1}} + \frac{T_{e3}}{G_{A1}G_{A2}} = 170 + \frac{28710}{10^4} + \frac{170}{10^4 \times 0.01} = 175 \text{ K}$$

$$F = 1 + \frac{T_e}{290} = 1 + \frac{175}{290} = 1.6 \equiv 2.04 \text{ dB} \quad \text{Achieves spec at lowest cost}$$