

ENEL 434 Electronics II

Lecture 7

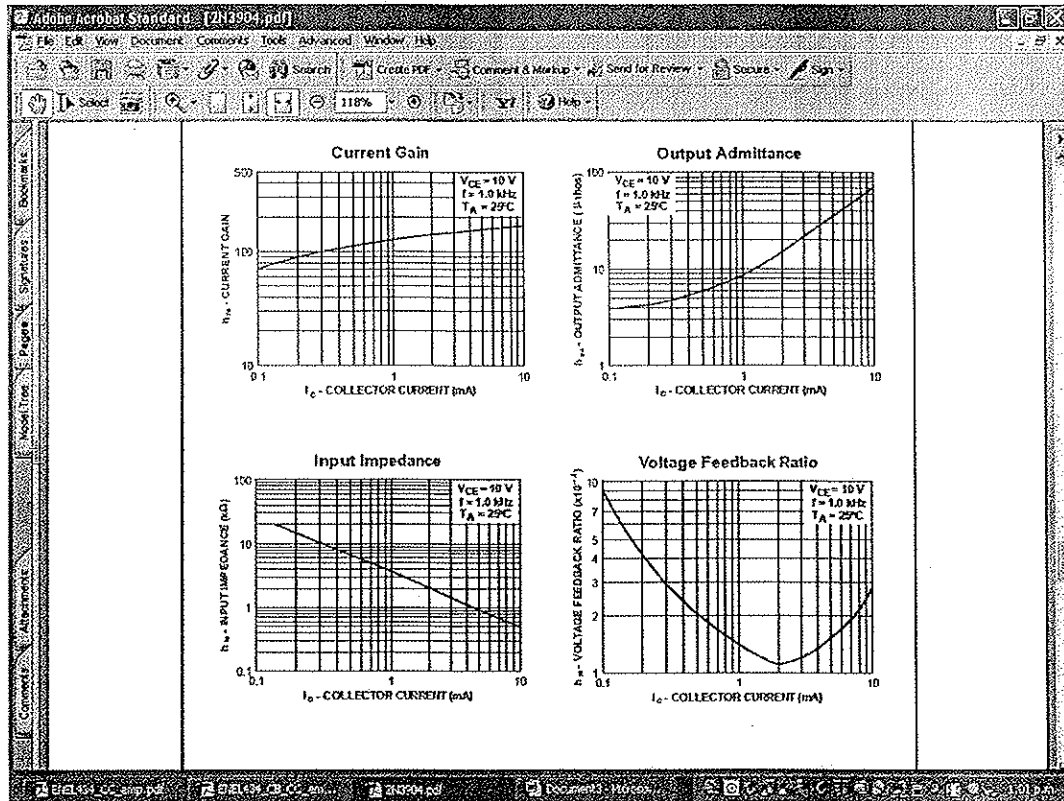


Fig 1 2N3904 h parameters.

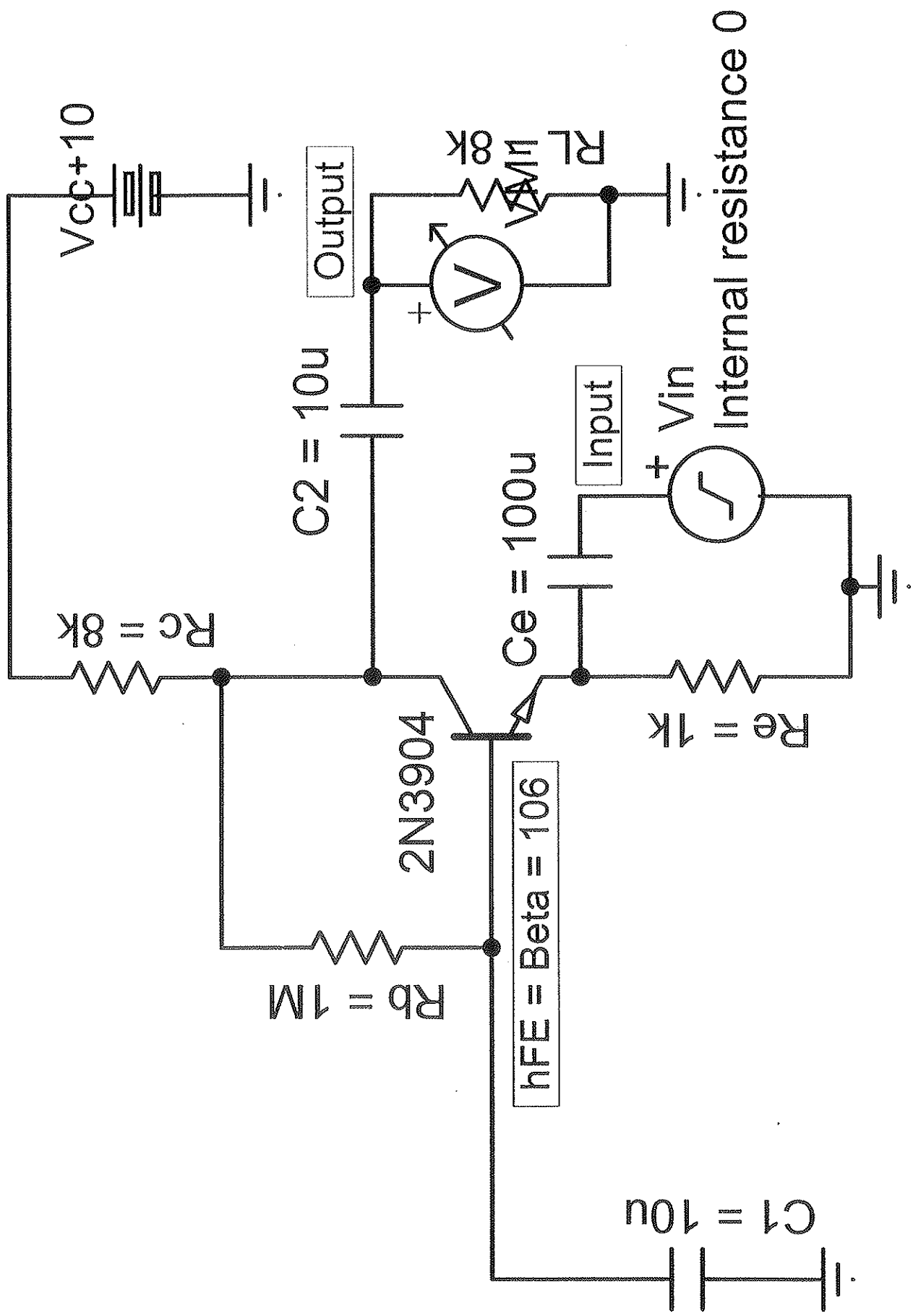


Fig 2. CB amplifier with collector to base bias.

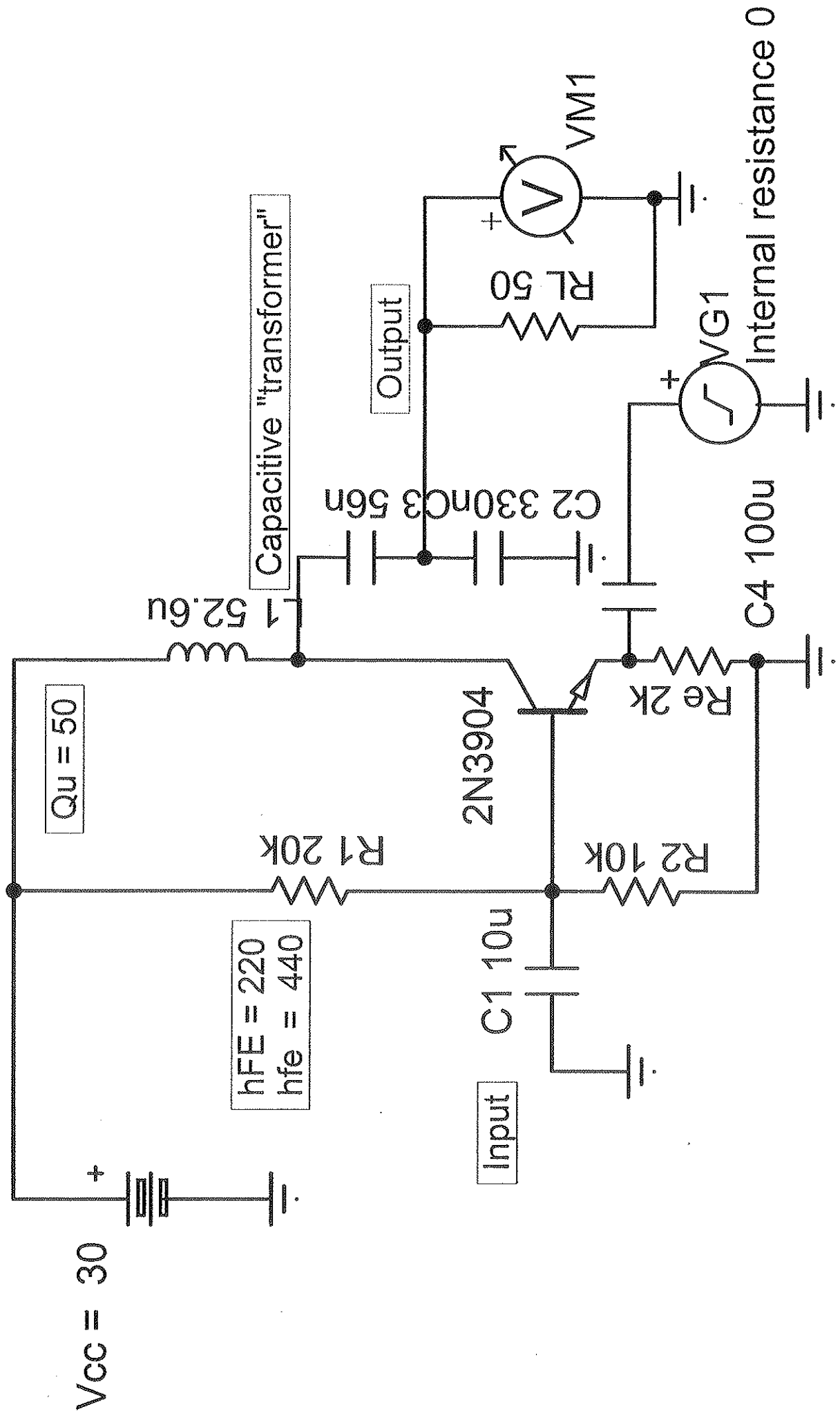


Fig 3 CB amplifier with tuned collector load

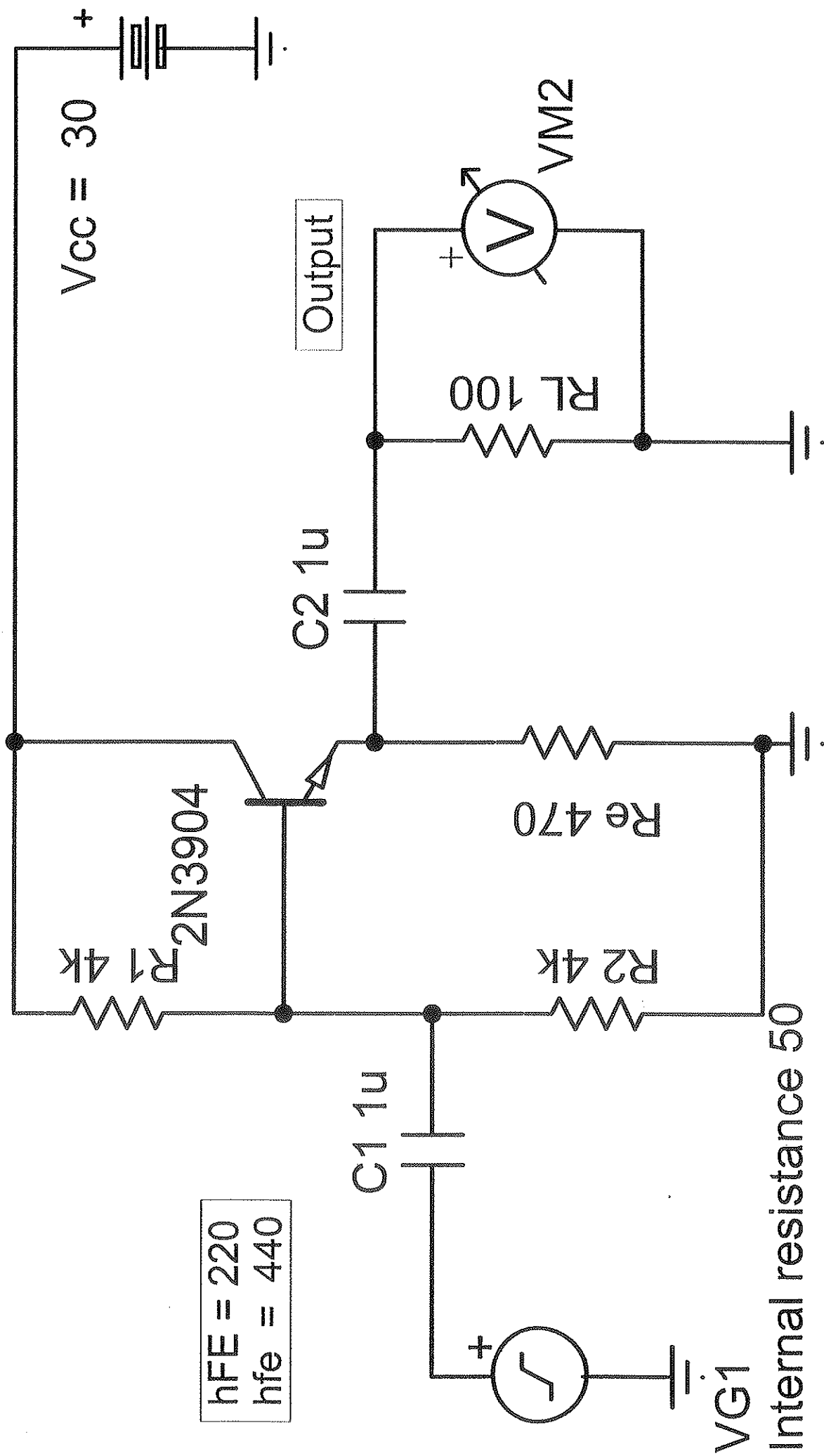


Fig 4 Common Collector amplifier


Review

Step by step design

- ① Find approx f_0 (ω_0)
- ② Insert R_{coil} (eq R_p).
- ③ (a) Change // to series.
(b) Change series to //
- ④ Collect together (in R) all the resistances. (check h_{oe})
- ⑤ Find peak gain at f_0 (check f_0 hasn't changed)
- ⑥ SS gain vs large signal gain.
- ⑦ f_{in}
- ⑧ C_E vs V_{CE} .
- ⑨ Make Cuts ~~(a) f_{in}~~ BJT.
- ⑩ Parameter stepping Temp.


Review - Quality factor Q

(A)

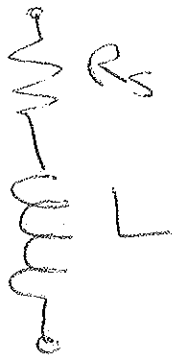


$$Q_s \equiv \frac{X_L @ f_0}{R_s}$$

(B)

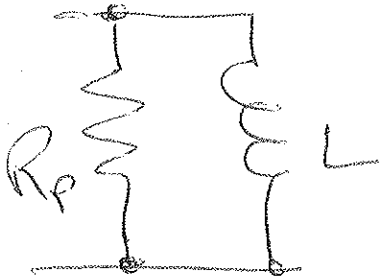


$$Q_p \equiv \frac{R_p}{X_L @ f_0}$$


(C)

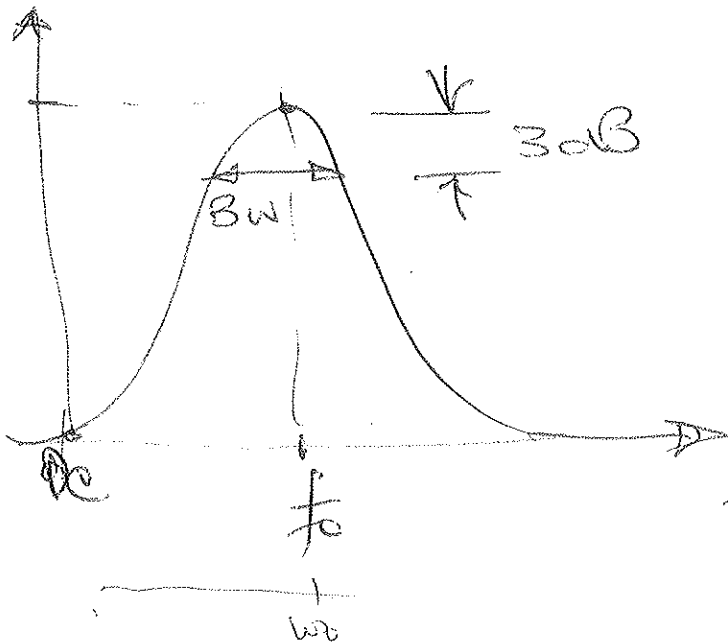


$$Q \equiv \frac{f_0}{BW}$$

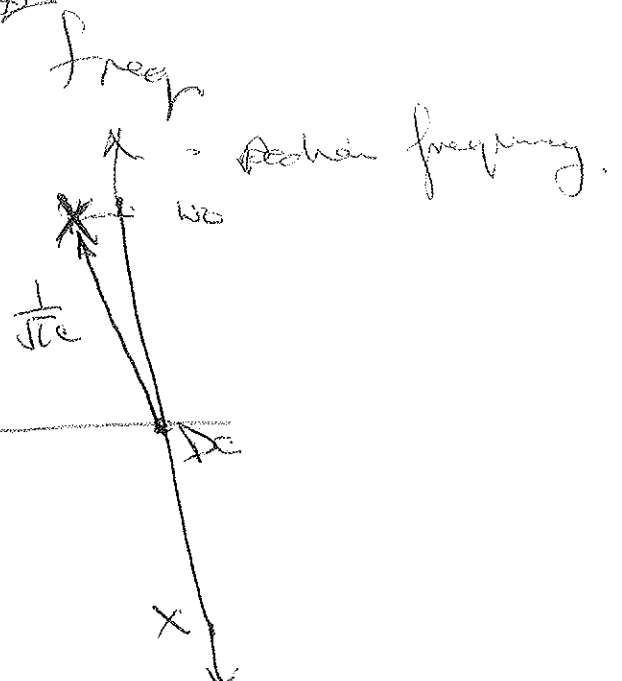

$$Q_u = 50$$

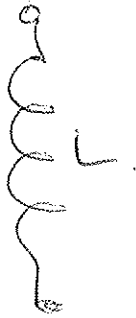

\approx

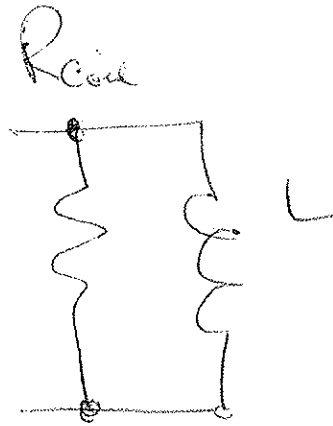

Not realistic
but math
convenient




$$Q_u = Q_{unloaded}$$

or



Realistic,
a coil with
series resistor

$$Q_u = 50$$

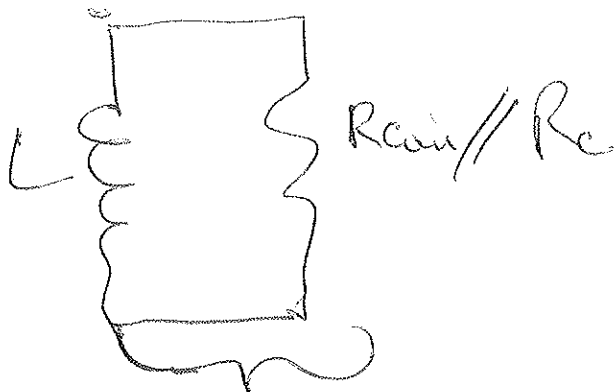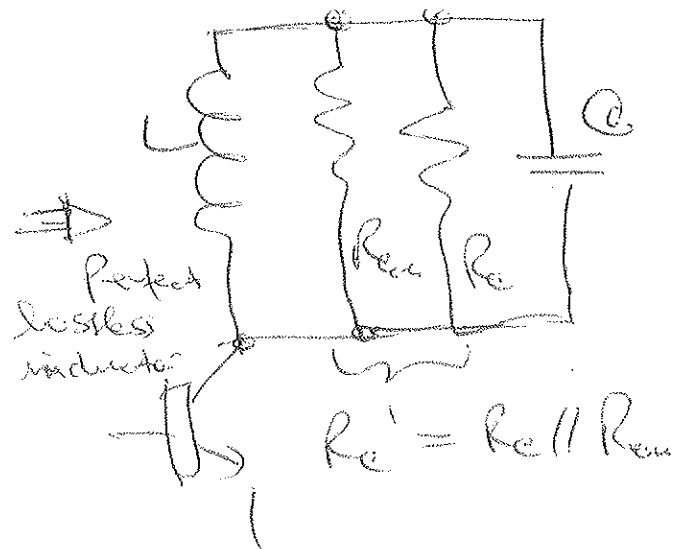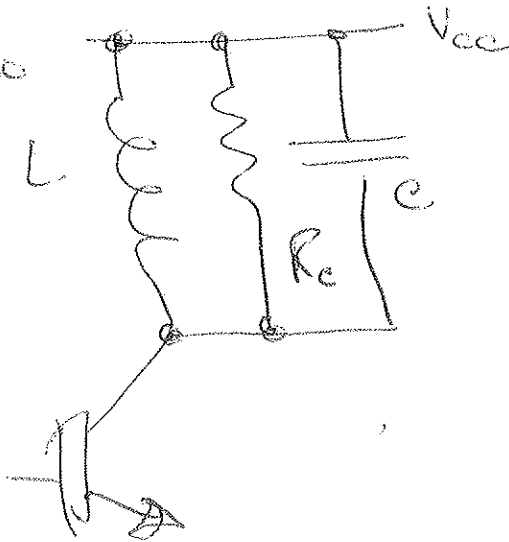

$$Q_{loaded} < Q_u$$