

ENEL434 Pop quiz

- 1) For the CE amplifier shown in Fig.1 find:
- The base current  $I_B$
  - The collector current  $I_C$
  - The voltage  $V_{CE}$
  - The emitter resistor  $r_e$
  - The small signal mid band gain  $|v_{out}/v_{in}|$
  - The input impedance at midband
  - The low frequency limit in Hz

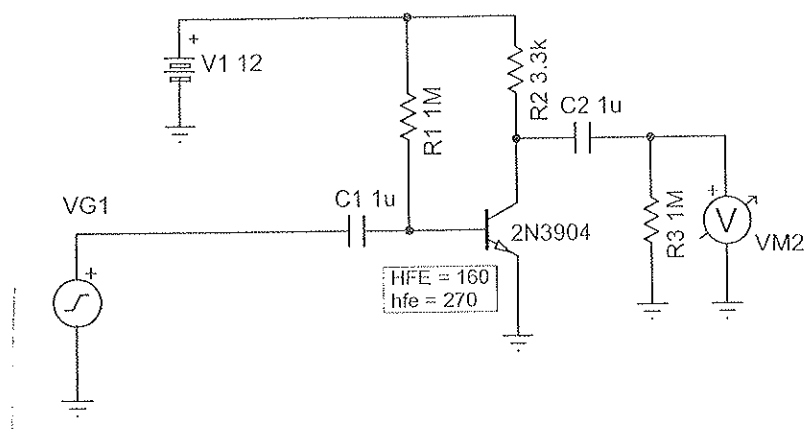


Figure 1. A truly dreadful CE amplifier

2 ) For the circuit shown in Fig.2 and using the Thevenin equivalent network for the base bias circuit, find

- $I_B$ ,
- $I_C$  and
- $V_{CE}$
- the small signal gain  $|v_{out}/v_{in}|$

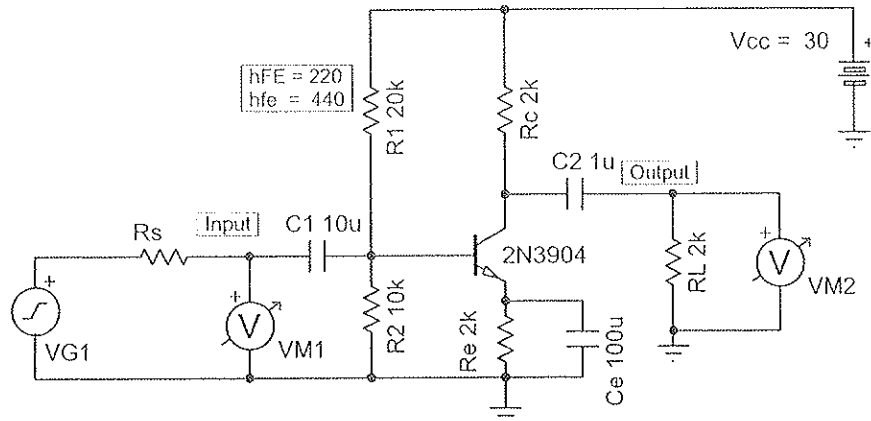


Figure 2. A well-biased CE amplifier

Answers to Pop Quiz EVEL 434  
Feb 2008

- ①
- (a)  $I_B = (12 - 0.7) / 10^6 = 11.3 \mu A$
  - (b)  $I_C = h_{FE} I_B = 160 \times 11.3 \times 10^{-6}$   
 $= 1.8 \text{ mA}$
  - (c)  $V_{CE} = 12 - 1.8 \times 10^{-3} \times 3.3 \times 10^3$   
 $= 6.06 \text{ V}$
  - (d)  $r_e = 0.026 / 1.8 \times 10^{-3} = 14.4 \Omega$
  - (e)  $A_{v(s)} = - \frac{3.3 \text{ k} \parallel 1 \text{ M}}{14.4} = -229$
  - (f)  $R_{in}(f > f_L) = 1 \text{ M} \parallel h_{FE} r_e$   
 $= 1 \times 10^6 \parallel 270 \times 14.4 \approx 3.9 \text{ k}\Omega$
  - (g)  $f_L = 1 / 2\pi \times 3.9 \times 10^3 \times 1 \times 10^{-6}$   
 $= 41 \text{ Hz}$

Probably none of these answers will be that precise since  $h_{FE}$  (or  $\beta$ ) and  $r_e$  vary over large spans.

More realistic answers

(a)  $I_B = 11.3 \mu A \pm 2 \mu A$

(b)  $I_C = 1.8 \text{ mA} \pm 2 \text{ mA}$

(c)  $V_{CE} = 6 \pm 1 \text{ V}$

(f)  $R_{in} = 4 \text{ k}\Omega \pm 1 \text{ k}\Omega$


(d)  $r_e = 14 \pm 2 \Omega$

(e)  $A_v = -225 \pm 25$

(g)  $f_L = 40 \pm 10 \text{ Hz}$

②

Answer to pop quiz

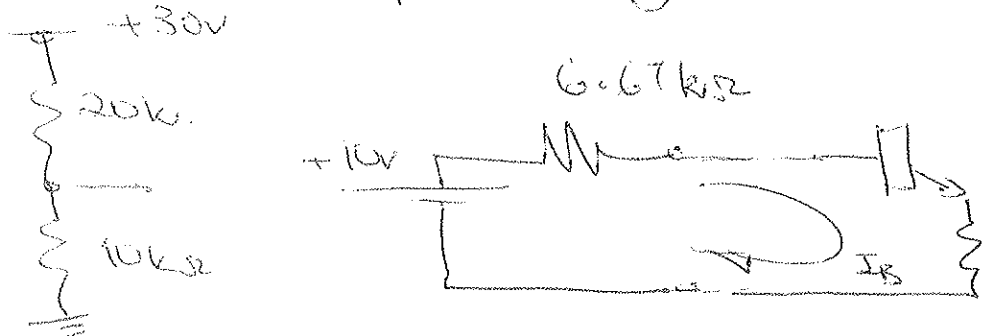

(a)  $V_{TH} = 10V$  ,  $R_{TH} = 6.67k\Omega$

$$10 - I_B \times 6.67 \times 10^3 - 0.7 - I_B \times 220 \times 2 \times 10^3 = 0$$

$$I_B = 9.3 / (6.67 + 440) \times 10^3$$

$$= 21 \mu A$$

(b)  $I_E = 4.6 mA$

(c)  $V_{CE} = 30 - 4.6 \times 10^{-3} \times 2 \times 10^3 - 4.6 \times 10^{-3} \times 2 \times 10^3$

$$= 11.6V$$

(d)  $A_{vss} = - \frac{2k // 2k}{r_e} / 5.7 = -175$