

EWEL 434

Lecture 6

B March 2008



Impedance Matching

This is needed when the actual load is not equal to the optimal load needed by the output transistor.

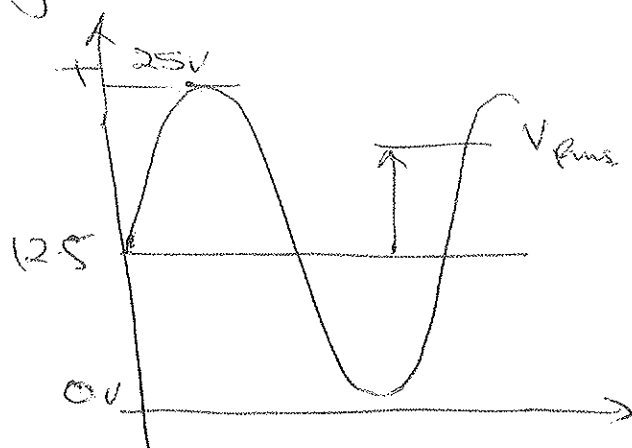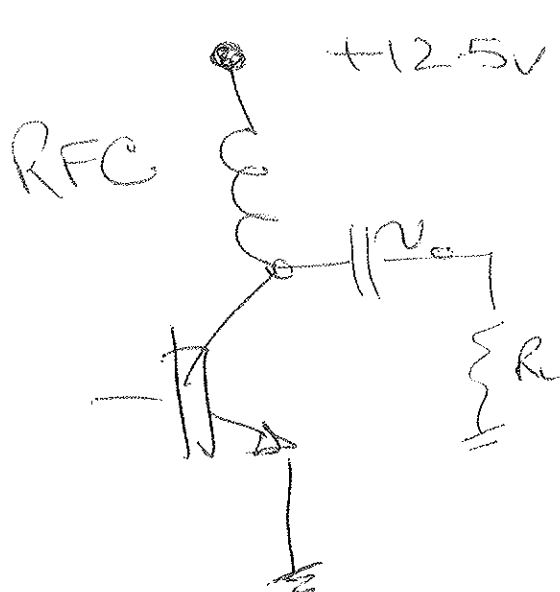Example Assume we have a 50Ω load.
(ie a $\lambda/2$ diode).

Power supply voltage = $12.5V$.



Max output power required = $26W$.
(limit of mobile regs).




$$V_{C_{rms}} = 8.84V$$

$$R_L = \frac{(8.84)^2}{26} \quad R_L = 3\Omega$$

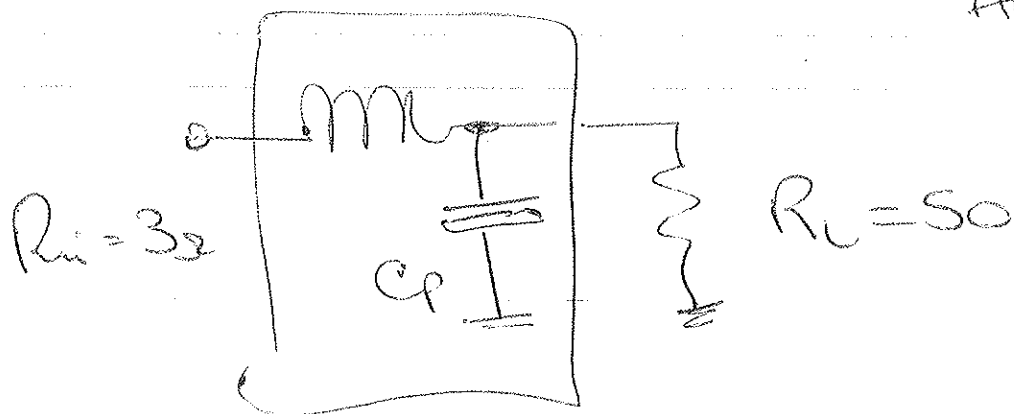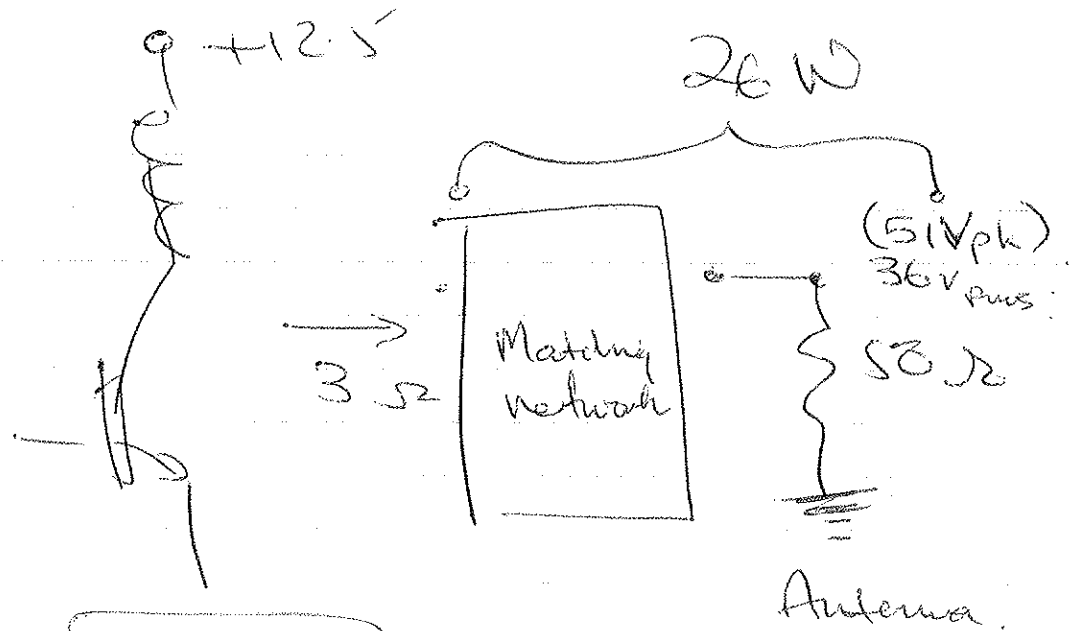At best. Since this assume $V_{CE(sat)} = 0$



Simple two pole L P F.

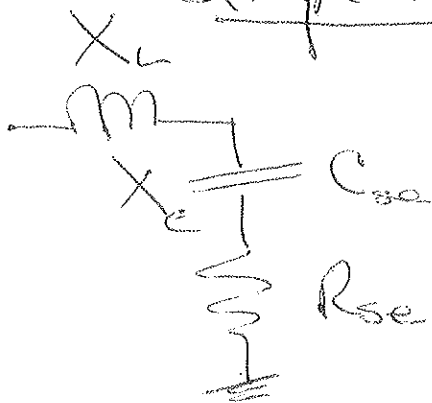

Assuming f_0 is known,
Choose a C_p so
that Q_p results in

$$R_{se} = 3\Omega$$



The resonant X_c with X_L
so that $R_{in} = 3\Omega$.

Example Choose $C_p = 253 \text{ pF}$


$$\therefore X_c = 12.6\Omega \quad \therefore Q_p = 4$$

$$\therefore R_{se} = 3\Omega \quad X_{cs} = -11.9\Omega$$

π matching networks.

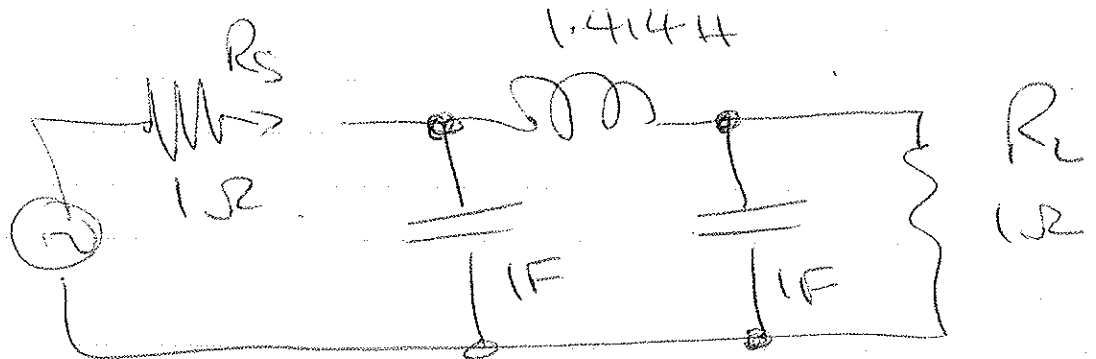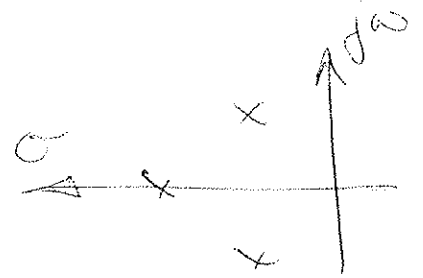


3 pole LPF Prototype ~~Diagram~~

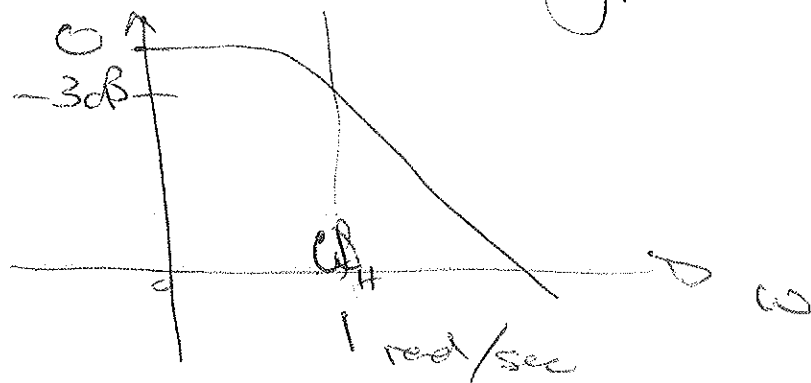


Scale to frequency.

Set $\omega_H = 10^7$
 $1.414 \times 10^{-7} H$



$f_H = 1.59 MHz$

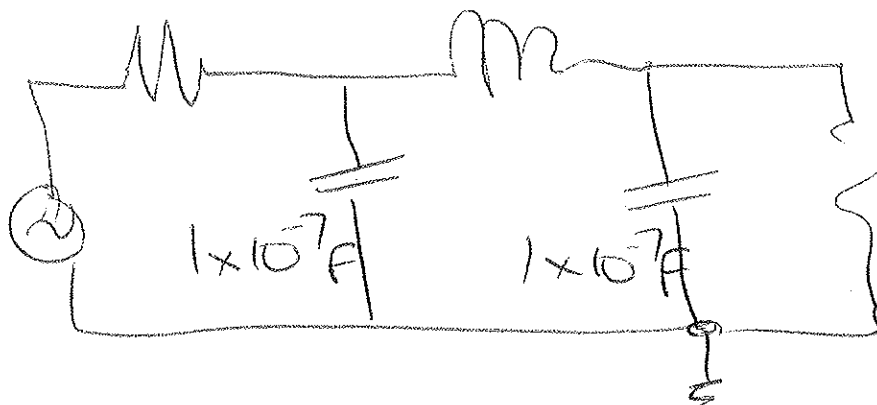

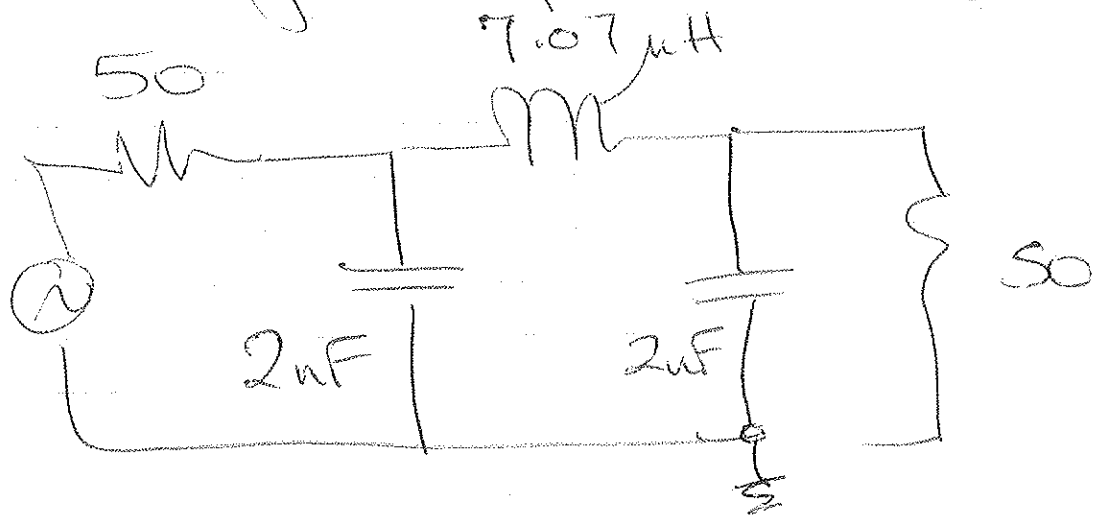Scale for impedances (say $R = 50\Omega$)



Have the impedances don't have to be equal.

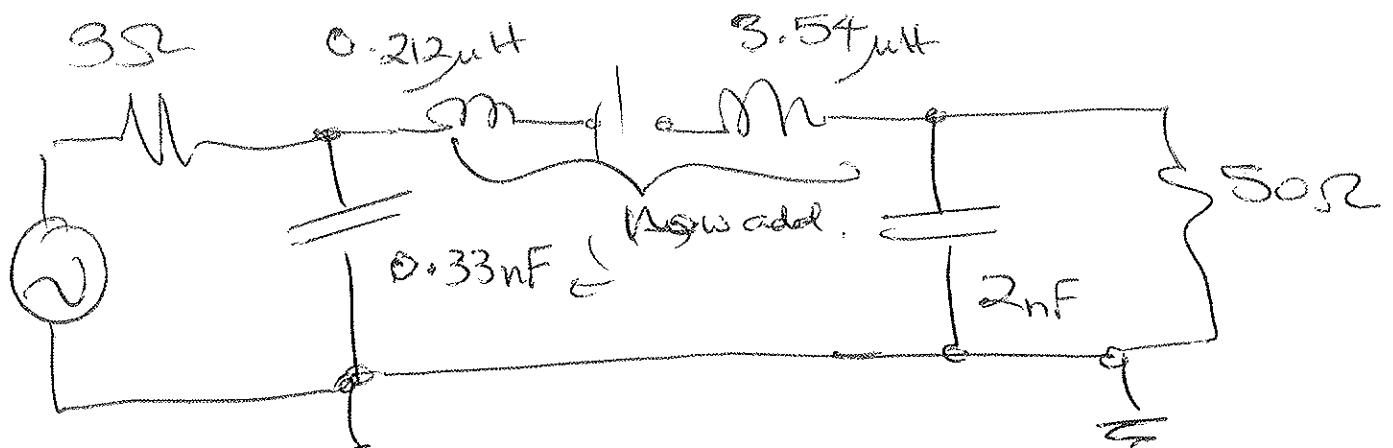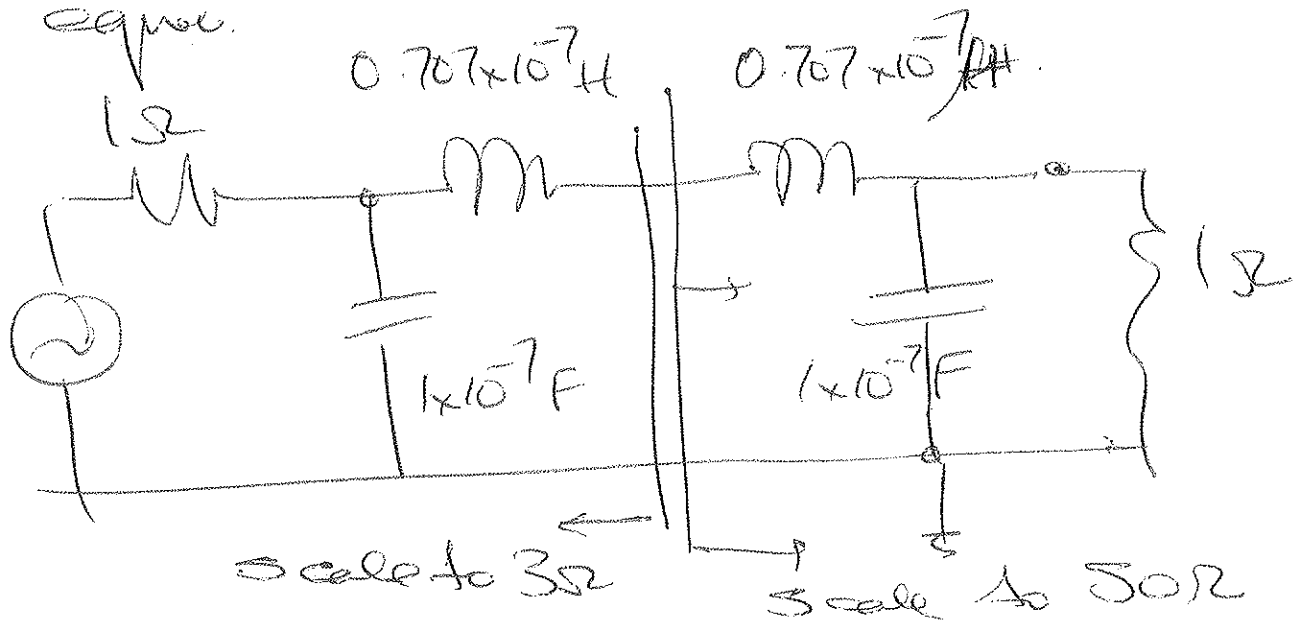

ENR 434


Electronics II

13 March 2006

Libre C

Fill in the gaps.

①

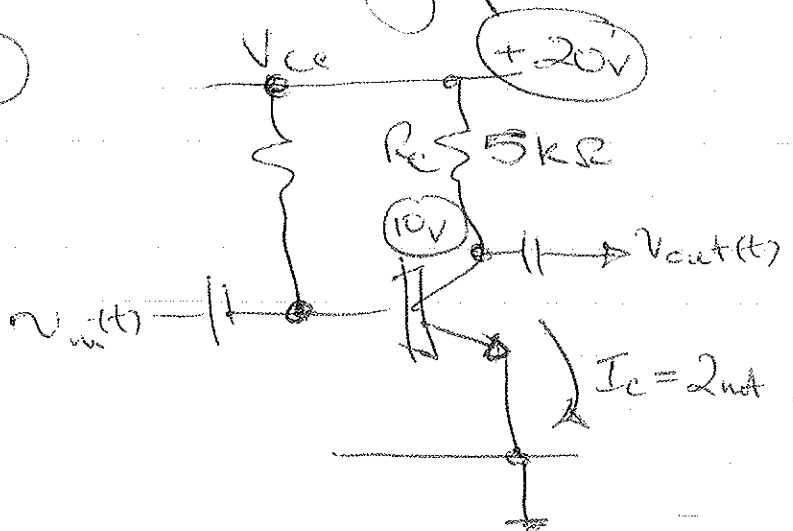


$$A_{v(ss)} = \frac{R_C}{r_e}$$

= -

= - x

= dB

②

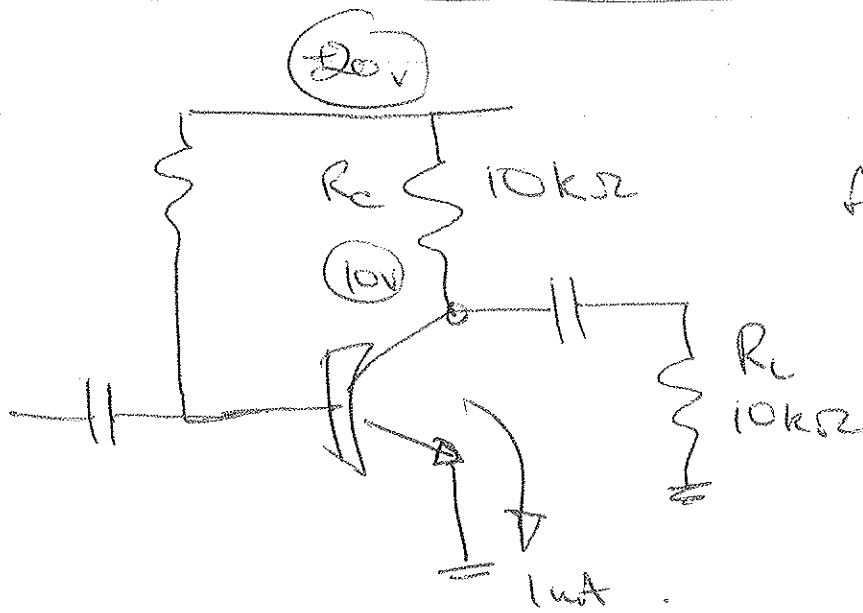


$$A_{v(ss)} = - \frac{R_C}{R_E \parallel r_e}$$

= -

= - x

= dB

3

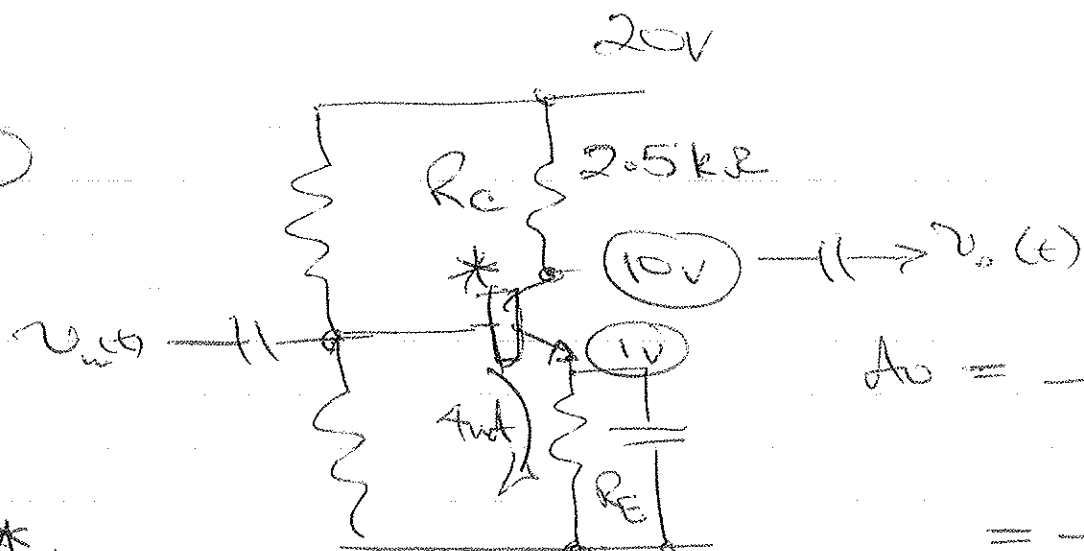

* $h_{oe} = 10 \mu S$

$r_o =$


$$A_v = - \frac{R_C \parallel R_L}{r_{eT}}$$

$=$

$=$

$=$ dB

4

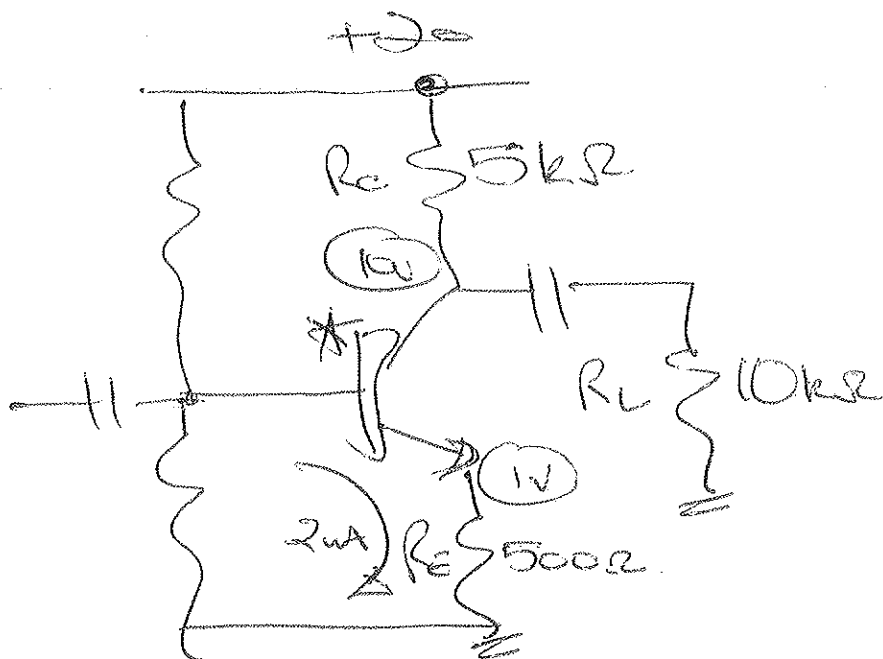

$h_{oe} = 100 \mu S$

$r_o =$

$$A_v = - \frac{R_C \parallel R_L}{r_e}$$

$=$

$=$

$=$

$=$

dB