



biosecurity

# ENEL 434 Electronics II


## Lecture 12

(3)

### Scattering parameters



3<sup>rd</sup> April


Two port  
scattering  
matrix

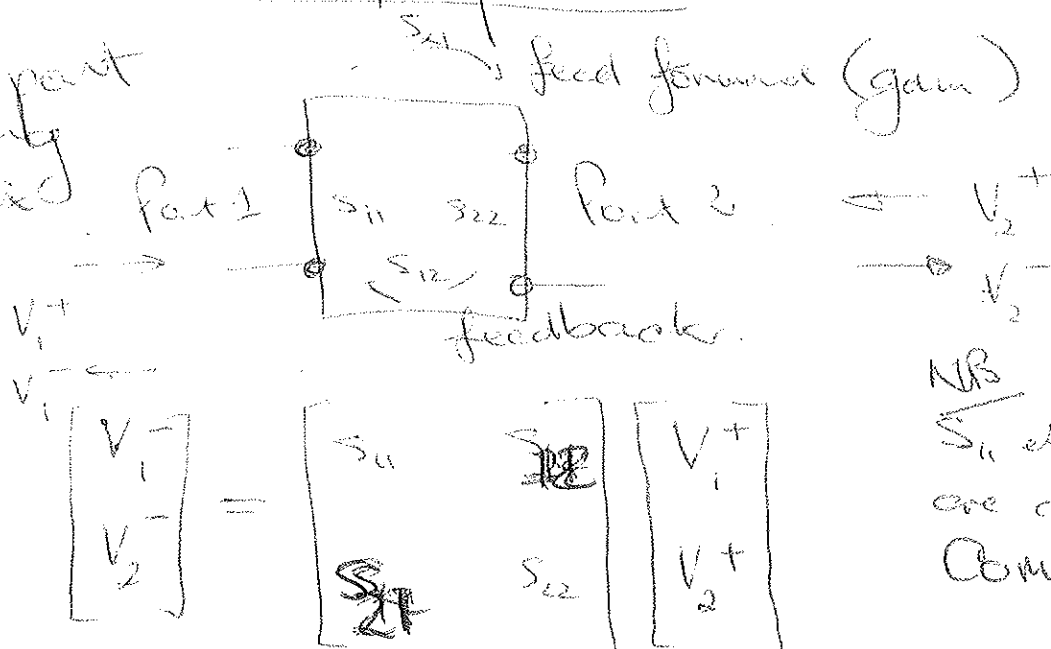

NB  
 $S_{11}$  etc  
are all  
COMPLEX


Recall  $\Gamma \equiv \frac{V^-}{V^+}$

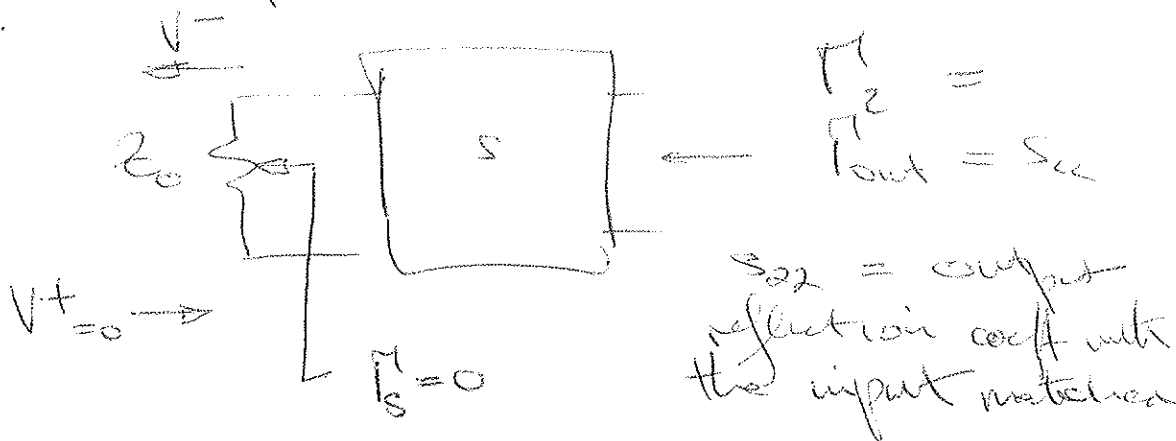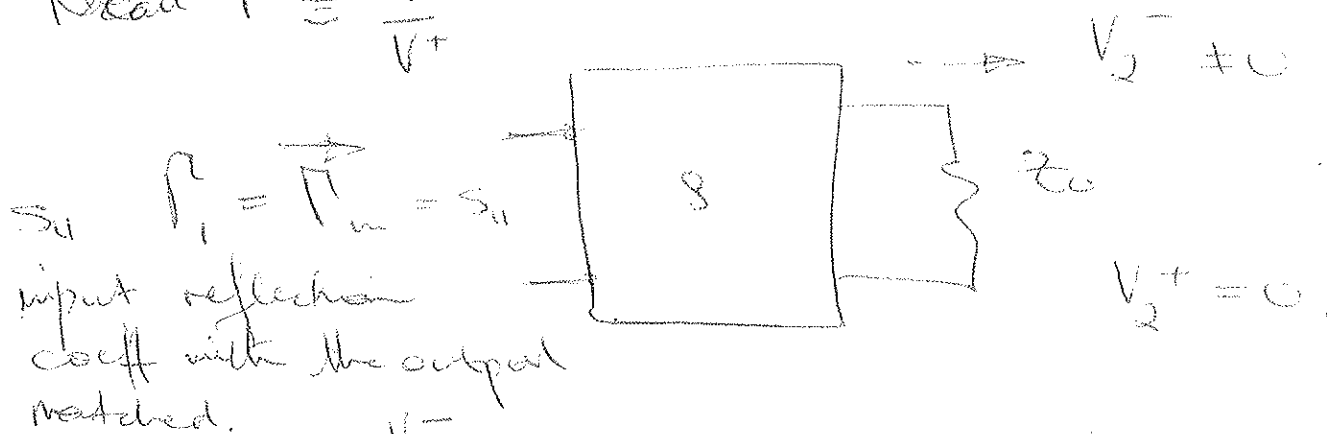

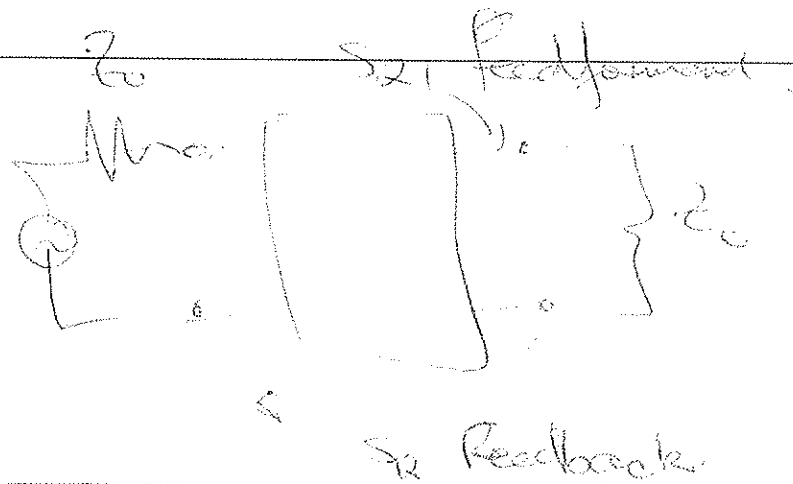

$$\Gamma_1 = \Gamma_{in} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \quad Z_L \neq Z_0$$
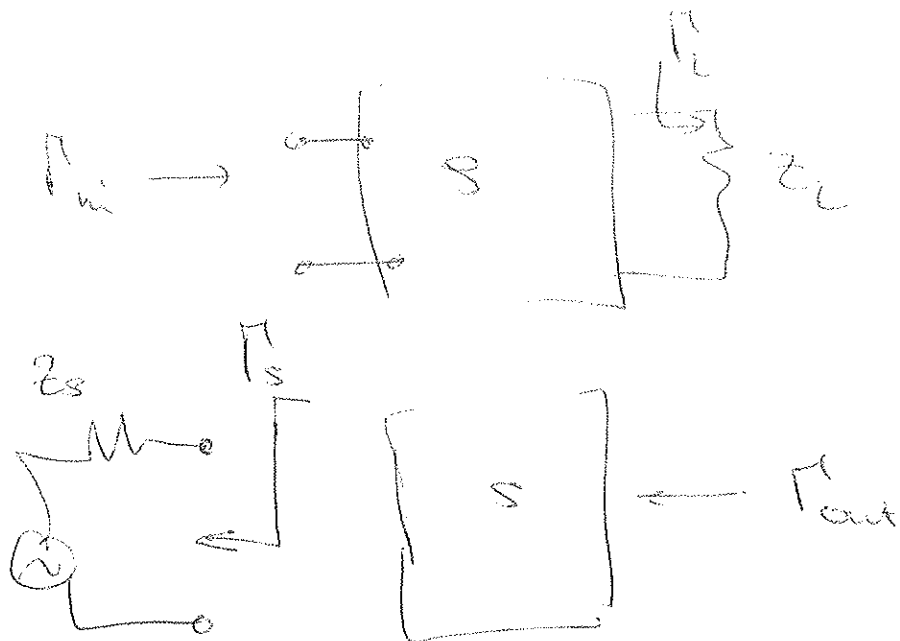
$$\Gamma_2 = \Gamma_{out} = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S} \quad Z_S \neq Z_0$$





©  $f = 4 \text{ GHz}$  (S)  
 $\lambda = 7.5 \text{ cm}$  in air  
 $\approx 5 \text{ cm}$  in a PCB or trace line.

Example If  
 $Z_0 = 50$

$$\begin{bmatrix} S_{11} = 0.12 \angle -116^\circ & S_{21} = 2.6 \angle 76^\circ \\ S_{12} = 0.03 \angle 51^\circ & S_{22} = 13 \angle -53^\circ \end{bmatrix}$$

(a) What is  $Z_{in}$  for  $Z_L = 50 \Omega$

If  $Z_L = 50 \Omega$ ,  $\Gamma_L = 0$

$$\Gamma_{in} = S_{11} + 0$$

$$= 0.12 \angle -116^\circ$$

$$\therefore Z_{in} = 0.21 - j0.6$$

$$\text{or } Z_{in} = 10.5 \Omega - j30 \Omega$$

(b) What is  $Z_{in}$  for  $Z_L = 10 \Omega + j50 \Omega$

$$\Gamma_L = 0.42 \angle 54^\circ \quad Z_L = 12 + j11$$

$$\Gamma_{in} = S_{11} + \frac{(S_{21} S_{12} \Gamma_L)}{(1 - S_{22} \Gamma_L)}$$

$$= 0.747 \angle -119^\circ \quad (\text{note: close to } S_{11})$$

(c) What is  $Y_{in}$  for  $Y_L = 25 \text{ mS} + j15 \text{ mS}$   
 $Y_0 = 1.25 + j0.75$   $Z_0 = 0.6 - j0.35$   
 Then  $Y_L$  in  $Z_L = 29 - j18 \Omega$  ✓

$$\therefore \Gamma_L = 0.33 \angle -127^\circ \checkmark$$


$$\Gamma_{in} = S_{11} + \frac{S_{21} S_{12} \Gamma_L}{1 - S_{22} \Gamma_L}$$


$$= 0.71 \angle -114^\circ \quad (\text{note: close to } S_{11})$$

$$Z_{in} = 0.22 \Omega - j 0.65$$

$$Y_{in} = 6.5 + j 1.4$$
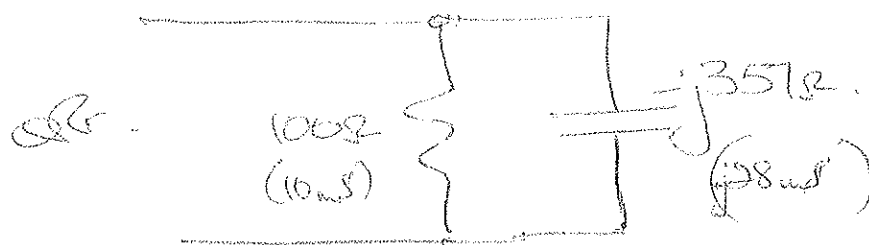
$$Y_{in} = 10 \text{ mS} + j 28 \text{ mS}$$



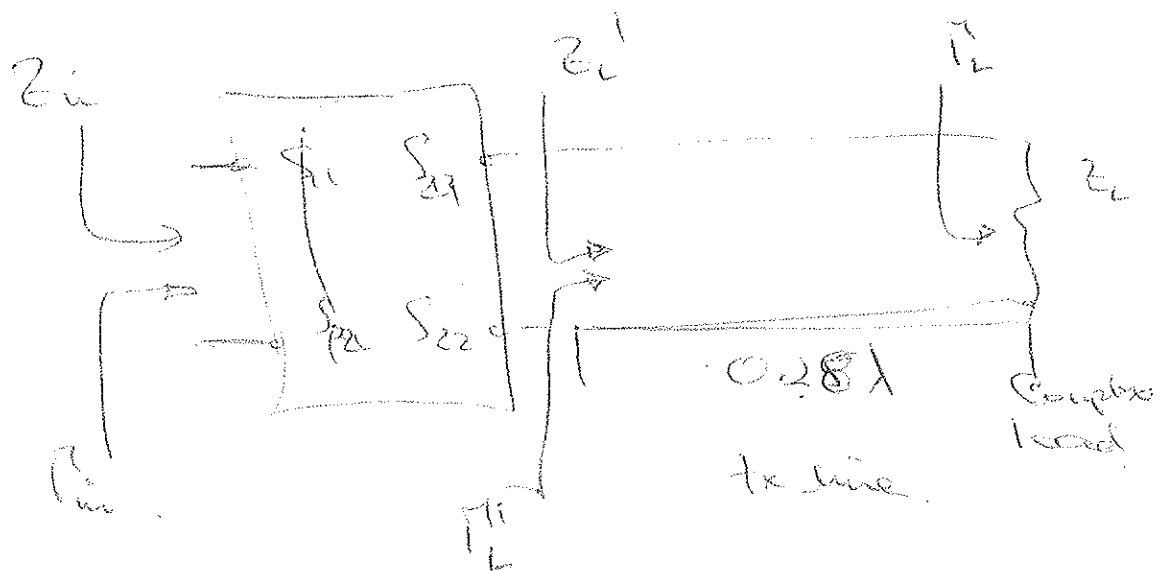

Summary

$$\Gamma_{in} = S_{11} + \frac{S_{21} S_{12} \Gamma_L}{1 - S_{22} \Gamma_L}$$

Special Cases

①  $Z_L = 50 \Omega$   $\Gamma_L = 0$

$$\Gamma_{in} = S_{11}$$

②  $Z_L = \infty$  or Open circuit  $\Gamma_L = 1$

$$\Gamma_{in} = S_{11} + \frac{S_{21} S_{12}}{1 - S_{22}}$$


③  $Z_L = 0$  or short circuit  $\Gamma_L = -1$

$$\Gamma_{in} = S_{11} - \frac{S_{21} S_{12}}{1 + S_{22}}$$

④  $S_{12}$  (feedback) = 0

Student Name.....Student ID.....ENEL434

## Smith Chart

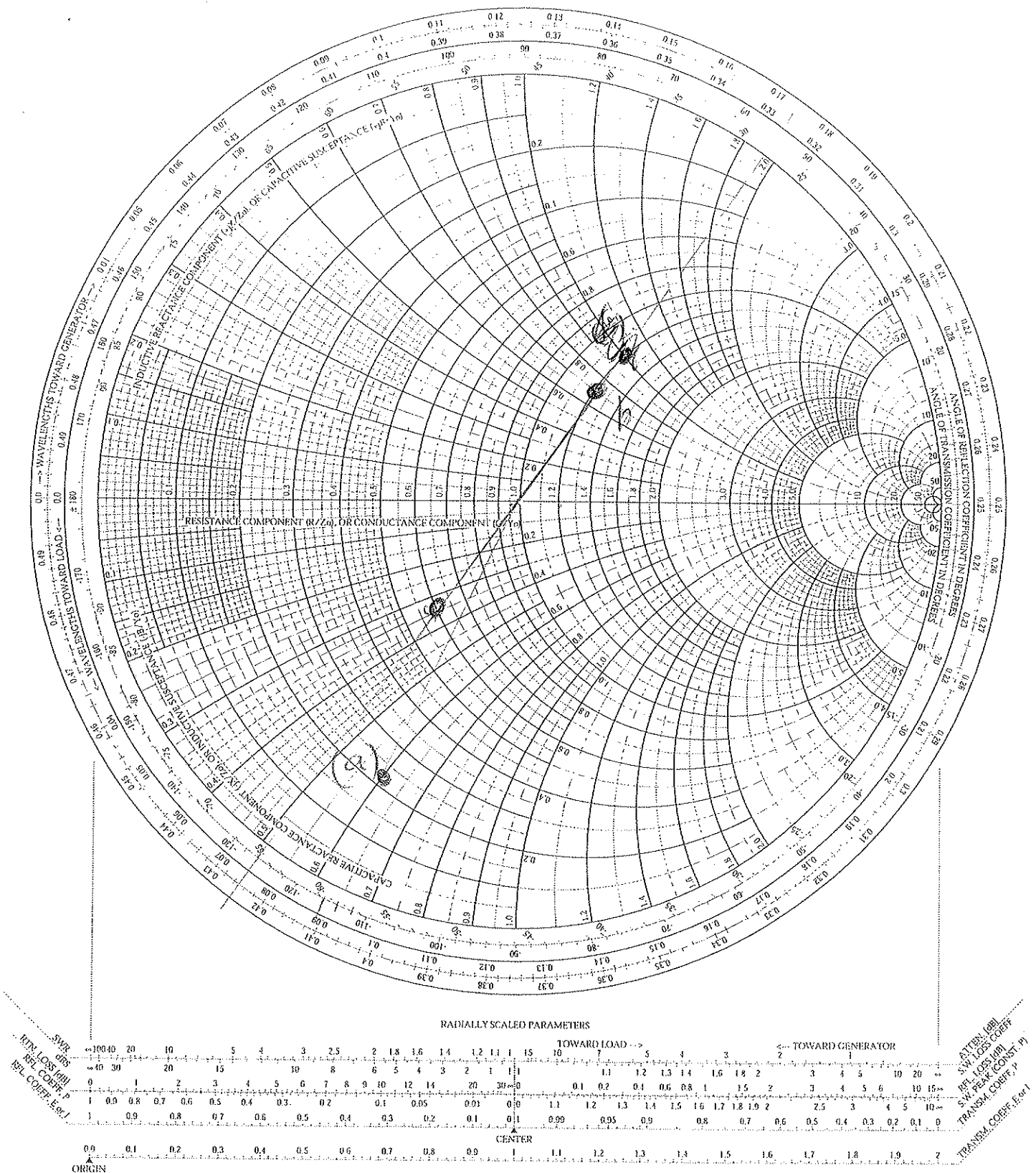

To be handed in with your answer booklet