



No marks homework. Answers

- 1) Find the equivalent capacitance; $C_{total} = 106 \text{ pF}$.
- 2) Find the resonant frequency $f_0 = 3.4 \text{ MHz}$.
- 3) Find the bandwidth $BW = 500 \text{ kHz}$.
- 4) Find the bias current; $I_C = 1.3 \text{ mA}$.
- 5) Find the output signal; $V_{out}(t) = 750 \text{ mV} \cdot \cos 2\pi 3.4\text{MHz } t \text{ v}$.
- 6) Find the input resistance $R_{in} @ f_0 = 130 \text{ ohms}$.
- 7) Find the power gain in dB $= 22 + 4 = 26 \text{ dB}$.
- 8) Find the efficiency; $\eta = 5.6\text{mW}/48\text{mW} \cdot 100 = 11.7 \%$.