

Smith Chart

Lecture 9

26th March



(1)

Uses

- ① Easy conversion between Z and Y
- ② Easy conversion between Z , Γ
- ③ Impedance matching with lumped components ("low" frequencies $< 500\text{MHz}$)
- ④ Impedance matching with transmission lines ("high" frequencies $> 500\text{MHz}$)



$$Z = R + jX = R - \cancel{j/\omega C}$$

(2)

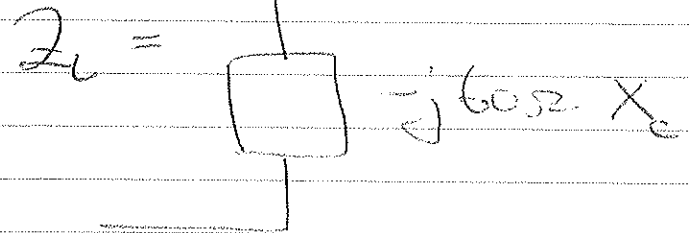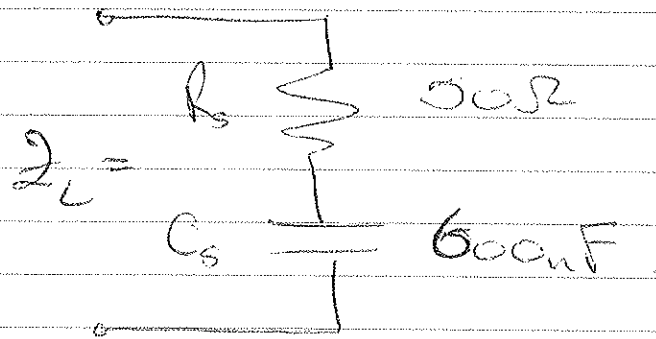

$$f_0 = 15.9 \text{ MHz}$$


Impedances

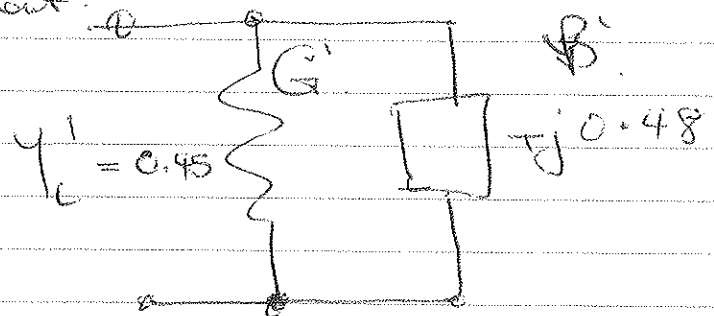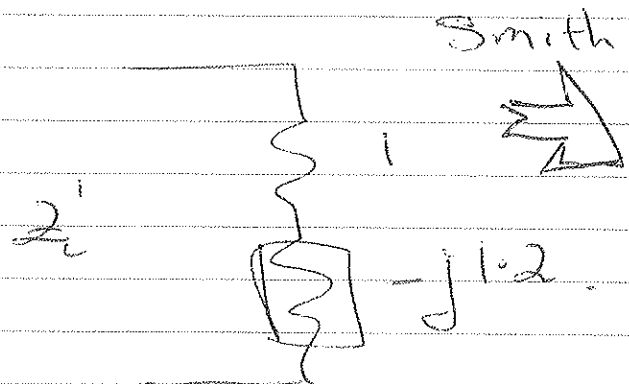

Add admittances

$$Y = G + jB$$

$$= \frac{1}{R_p} + j\omega C$$

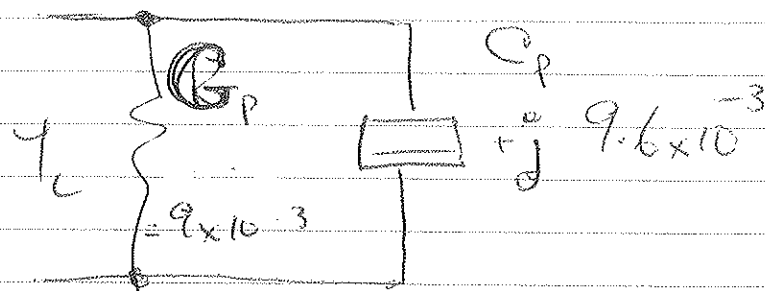

$$10 \times C = 9.6 \times 10^{-3}$$


$$\therefore C_p = 96 \text{ pF}$$

$$R_p = 110 \Omega$$

201



Student Name.....Student ID.....ENEL434

Smith Chart


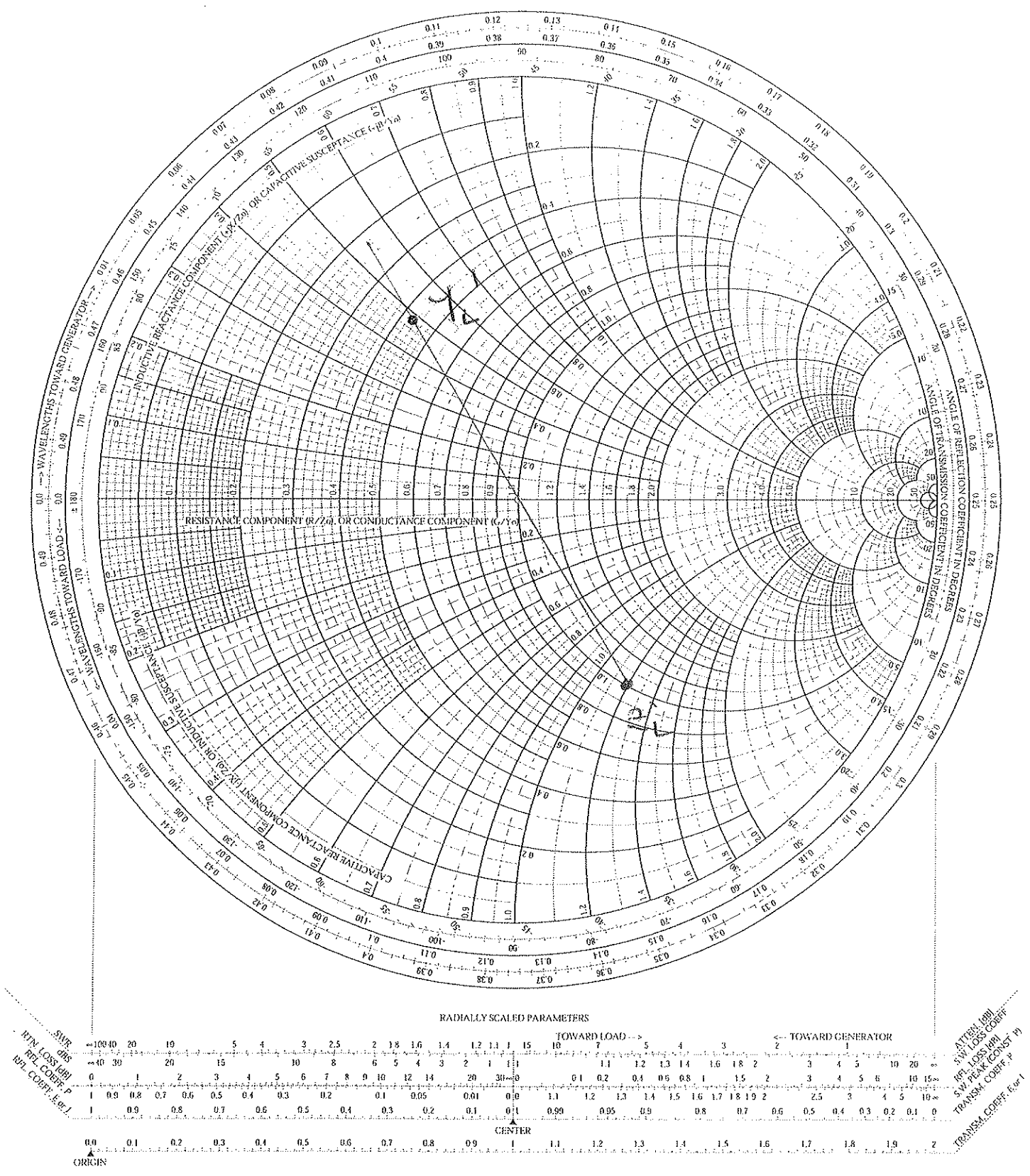


To be handed in with your answer booklet

3

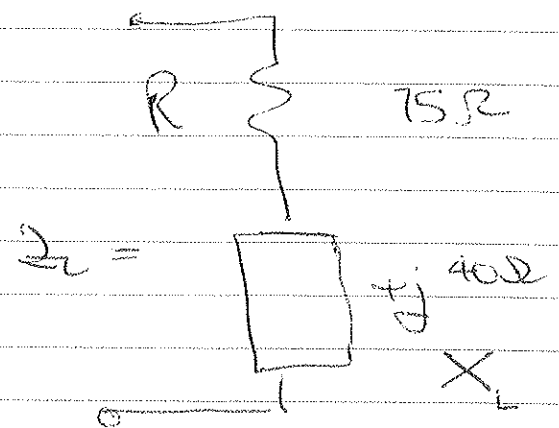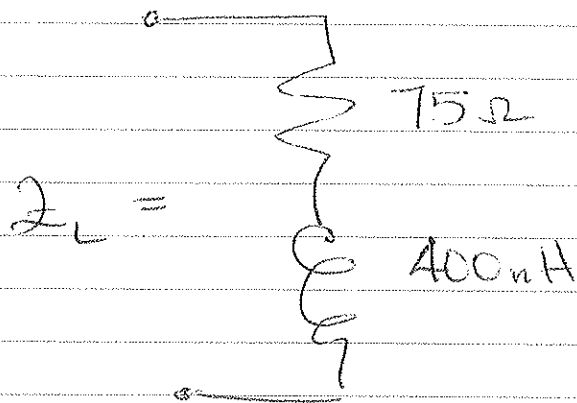

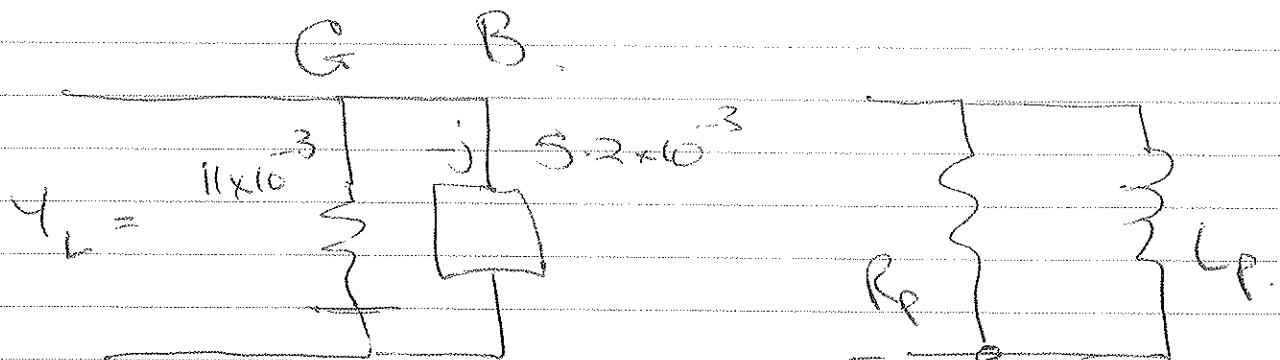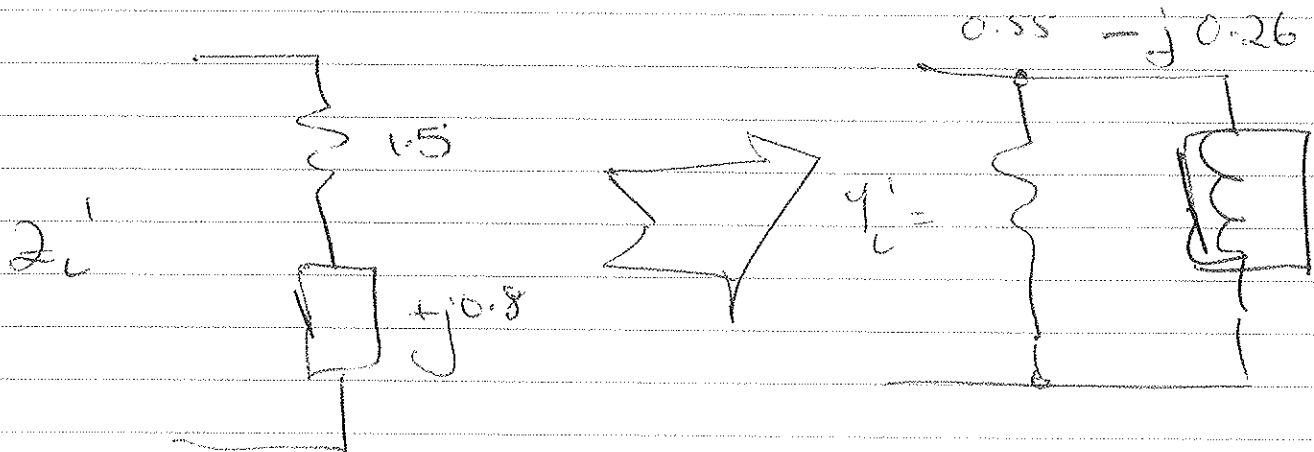$f_0 = 15.9 \times 10^6 \text{ Hz}$ $\omega_0 = 10^8$



$R_p = 90 \Omega$


$L_p = \cancel{10.9 \mu H} \cdot 1.9 \mu H$

$5.2 \times 10^3 = \frac{1}{10^8 L}$

$L = \frac{1}{10^8 \times 5.2 \times 10^3}$



Student Name.....Student ID.....ENEL434

Smith Chart

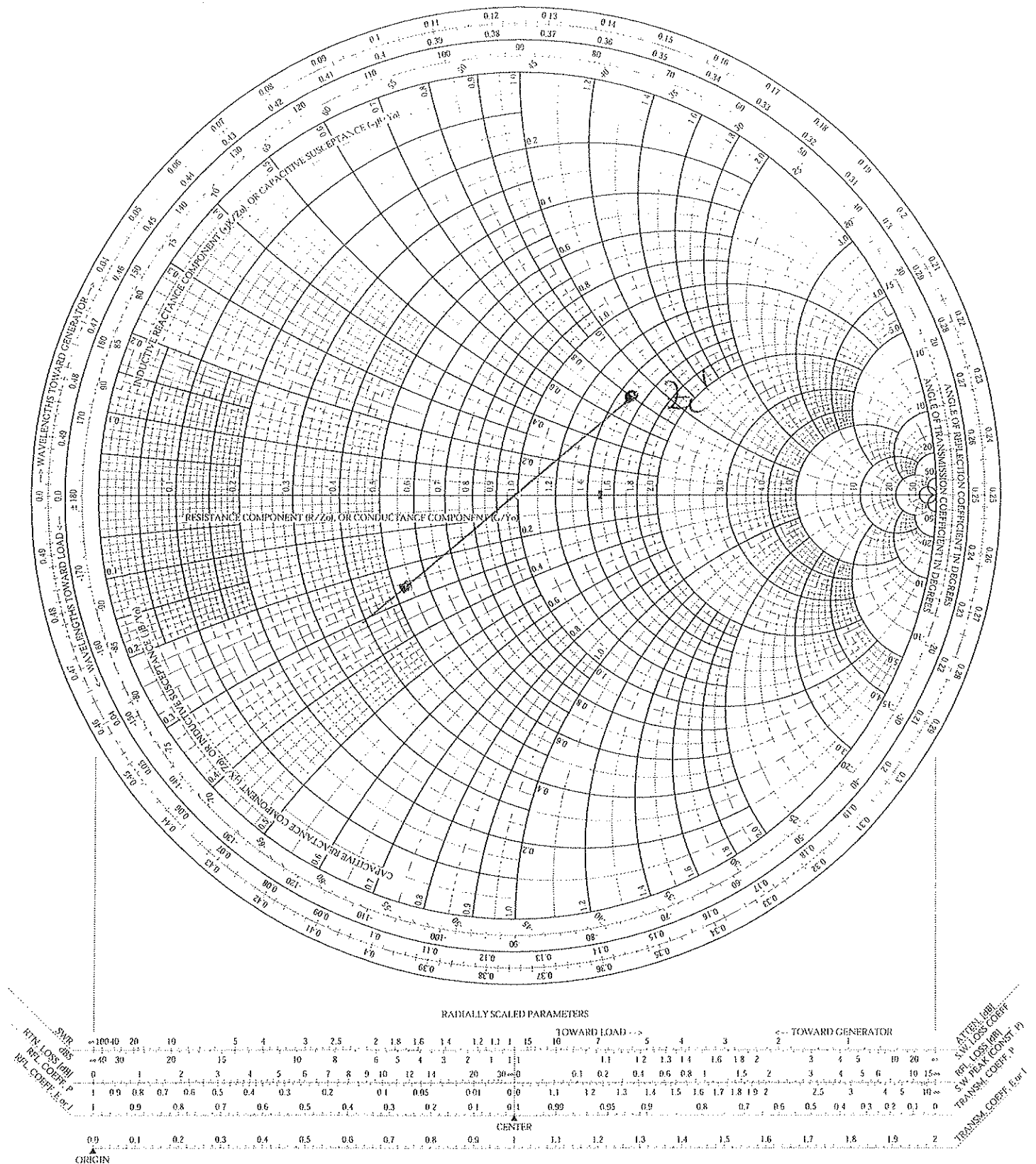

To be handed in with your answer booklet

② Reflection Coeffs.

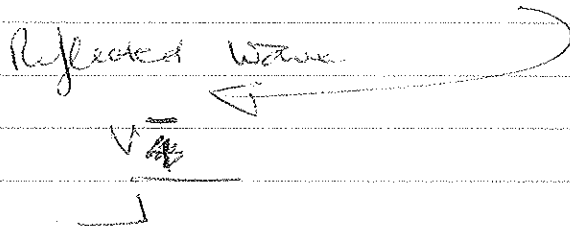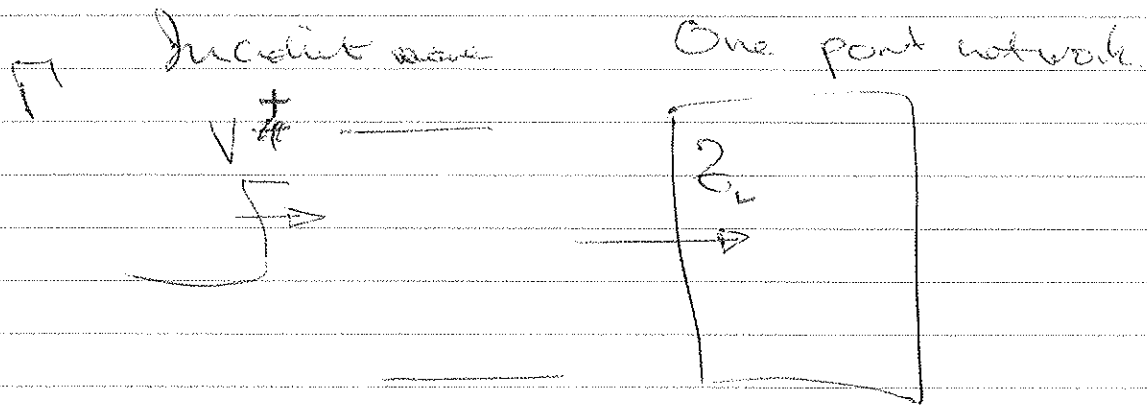

$$\Gamma \equiv \frac{V^-}{V^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

= $\frac{\text{Reflected wave amplitude}}{\text{Incident wave amplitude}}$

① Let $Z_L = 50 \Omega$ and $Z_0 = 50 \Omega$.

$$\Gamma_{sc} = 0$$


② Let $Z_L = \infty$ i.e. ∞ .

$$\Gamma_{oc} = \frac{1 - Z_0/Z_L}{1 + Z_0/Z_L} = 1 \angle 0^\circ$$

③ Let $Z_L = 0$ i.e. 0 .

$$\Gamma = \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} = -1 = 1 \angle 180^\circ$$

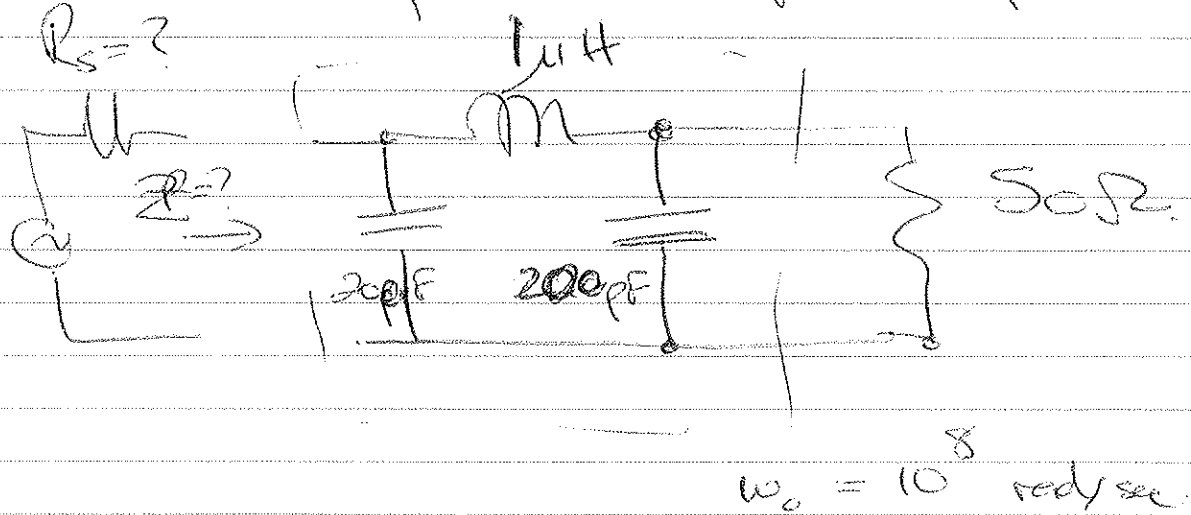③ Impedance Matching with Impedance Component



Step 1 Convert to impedances = (Res and React)